

MP309

Experiment 7

RC Differentiator and Integrator

Name :- Patel Mihir Hemantkumar

Roll no. :- I18PH037

Part 1 :- RC Integrator



Figure 1: Oscilloscope



Figure 2: Oscilloscope Probe

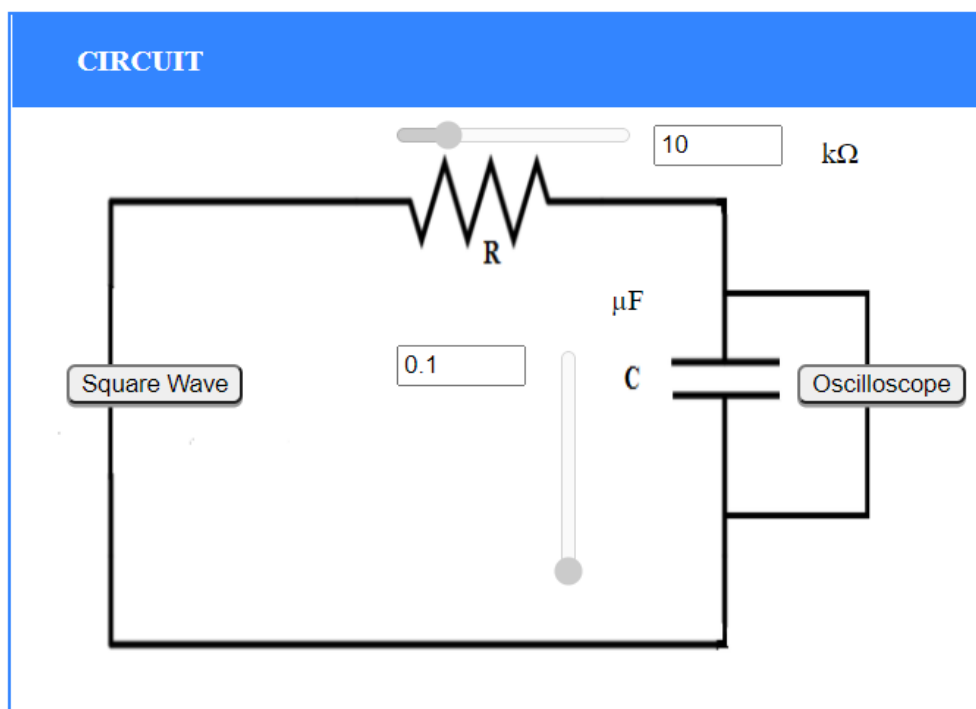


Figure 3: RC Integrator Circuit

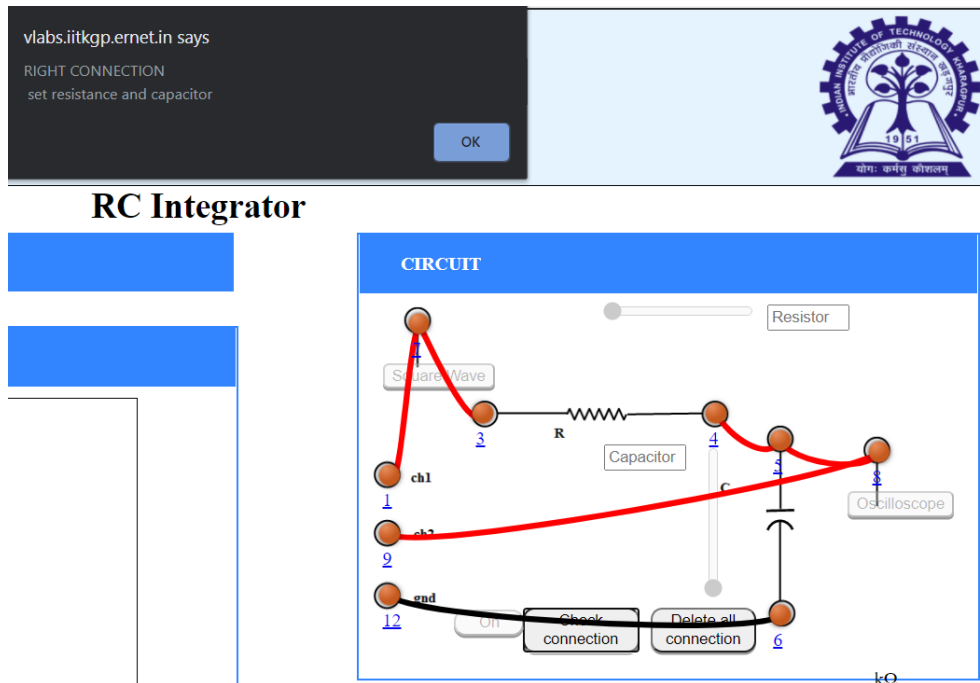


Figure 4: RC Integrator Circuit Connections

Initial Parameters :-

- Resistance(R) = $10\text{ k}\Omega$
- Capacitance(C) = $0.1\text{ }\mu\text{F}$

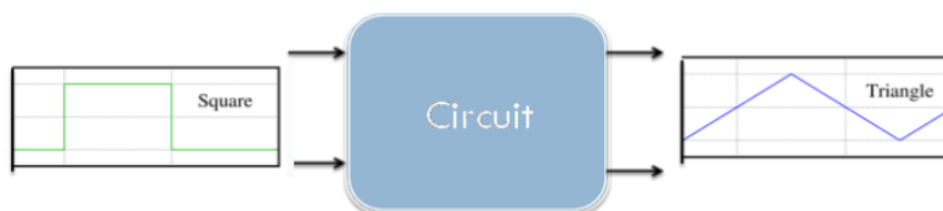


Figure 5: The Integrator is a circuit that converts or 'integrates' a square wave input signal into triangular waveform output.

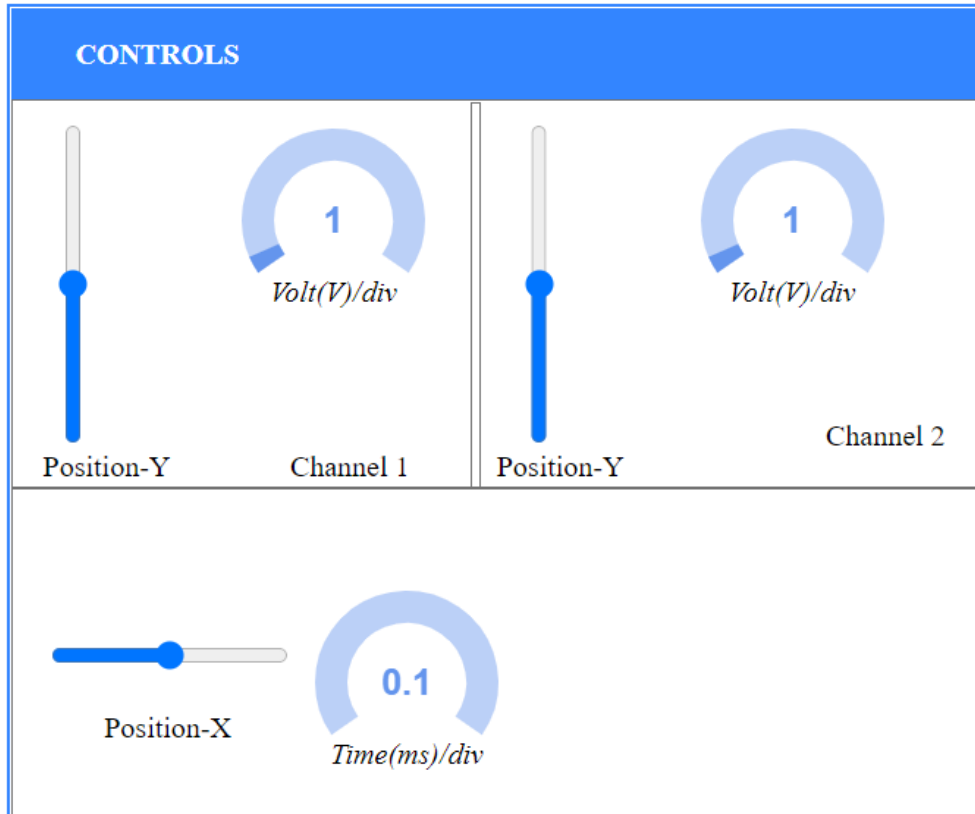


Figure 6: Controls

Oscilloscope

- * Channel 1(Input):
- * Channel 2(Output):

Figure 7: Oscilloscope Channel representation



Figure 8: Square Wave at Frequency = 1000

Frequency = (1 / Time Period)

Time Period = (1 / frequency)

i.e. Time Period = (1 / 1000) = 1msec

Amplitude (Volt/div) = 1 V

Time(ms)/div = 0.1 ms



Figure 9: Square Wave at Frequency = 2000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{i.e. Time Period} = (1 / 2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 10: Square Wave at Frequency = 3000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{i.e. Time Period} = (1 / 3000) = 0.333\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

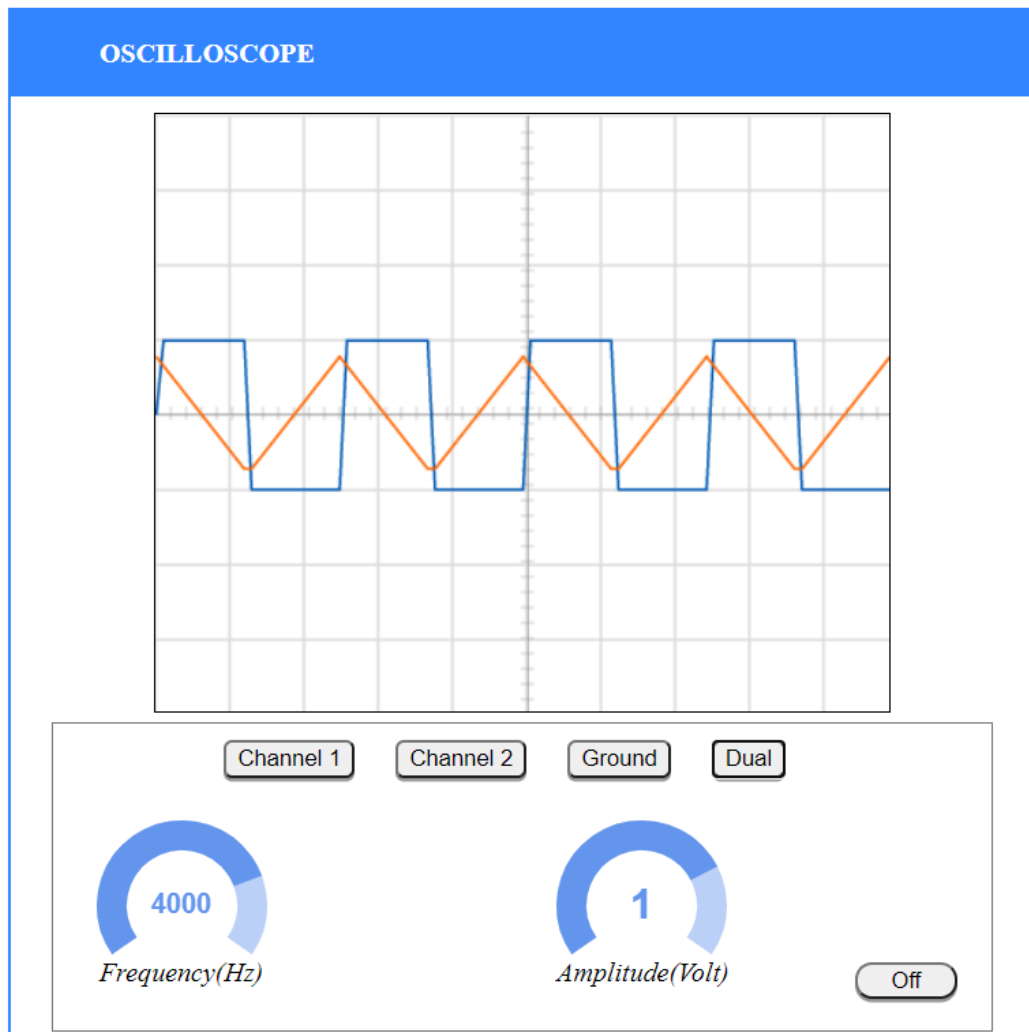


Figure 11: Square Wave at Frequency = 4000

Frequency = (1 / Time Period)

Time Period = (1 / frequency)

i.e. Time Period = (1 / 4000) = 0.25msec

Amplitude (Volt/div) = 1 V

Time(ms)/div = 0.1 ms

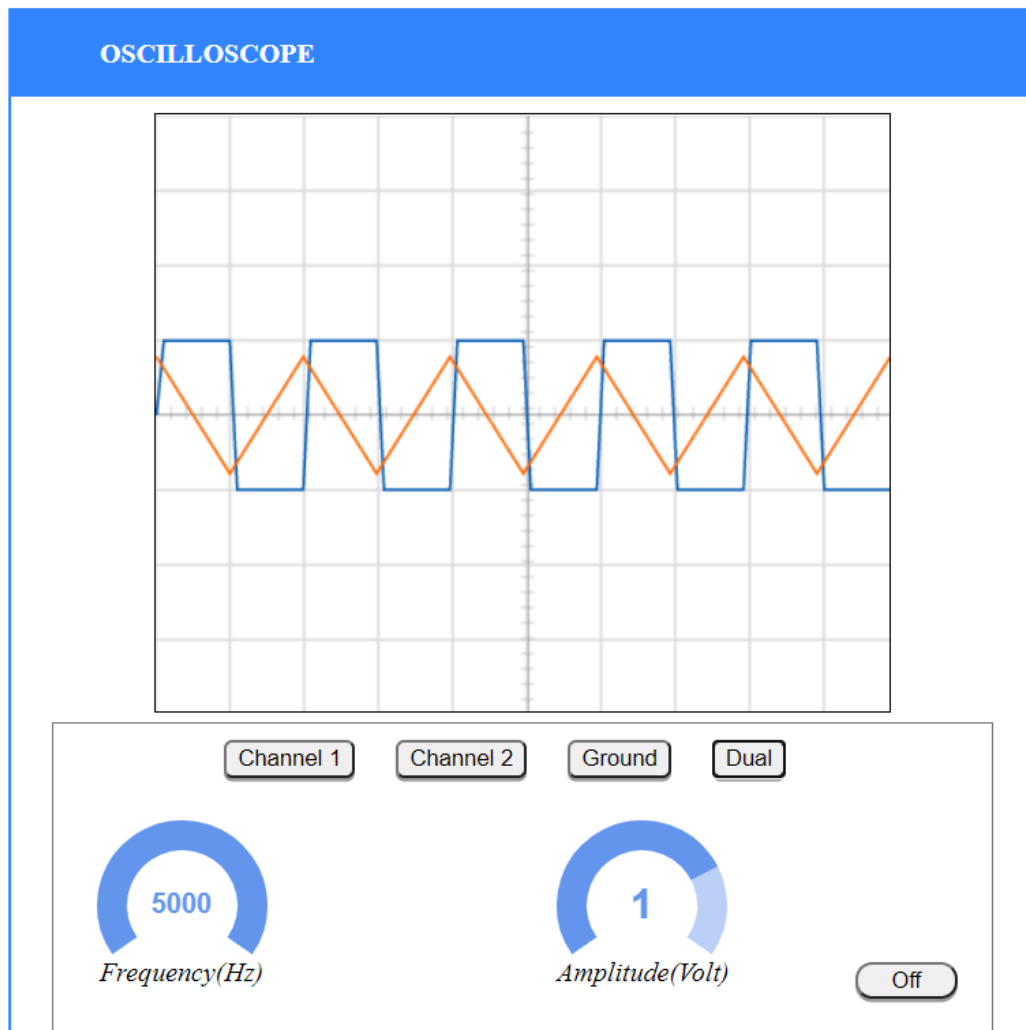


Figure 12: Square Wave at Frequency = 5000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{i.e. Time Period} = (1 / 5000) = 0.2\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

Part 2 :- RC Differentiator


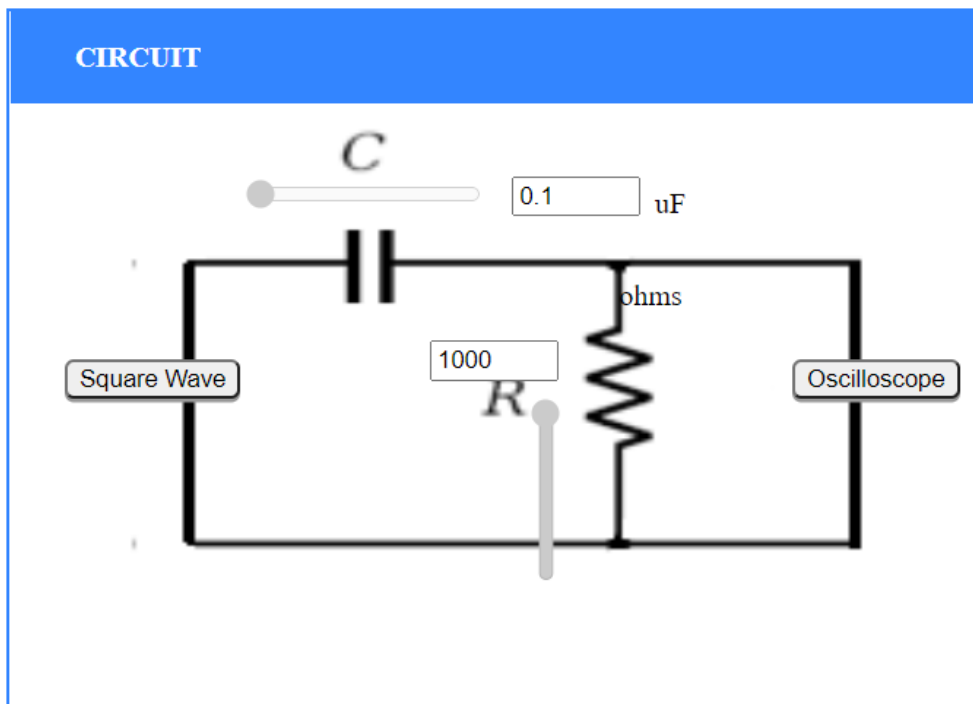


Figure 1: RC Differentiator Circuit

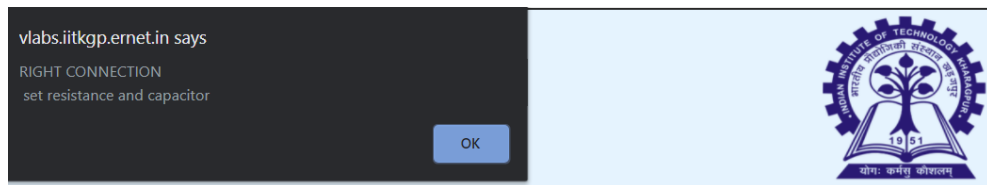

RC Differentiator

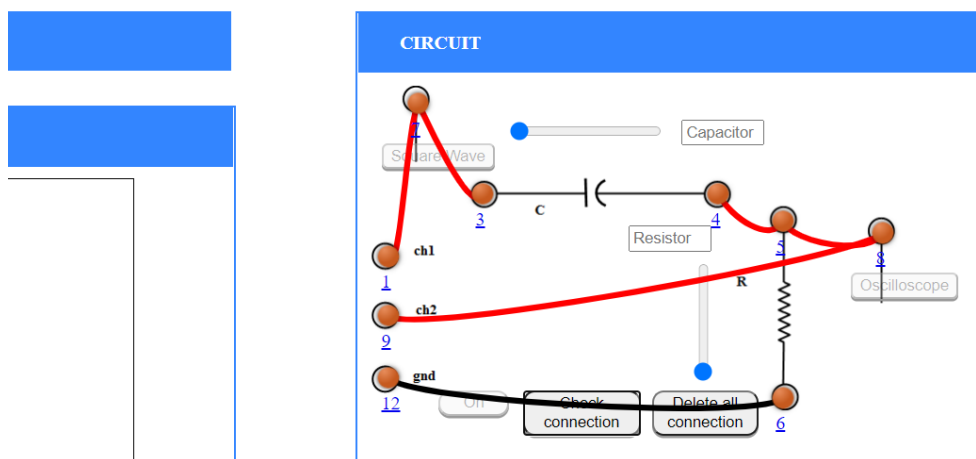


Figure 2: RC Differentiator Circuit Connections

Initial Parameters :-

- Resistance(R) = $1\text{ k}\Omega$
- Capacitance(C) = $0.1\text{ }\mu\text{F}$



Figure 3: The Differentiator circuit converts or 'differentiates' a square wave input signal into high frequency spikes at its output.

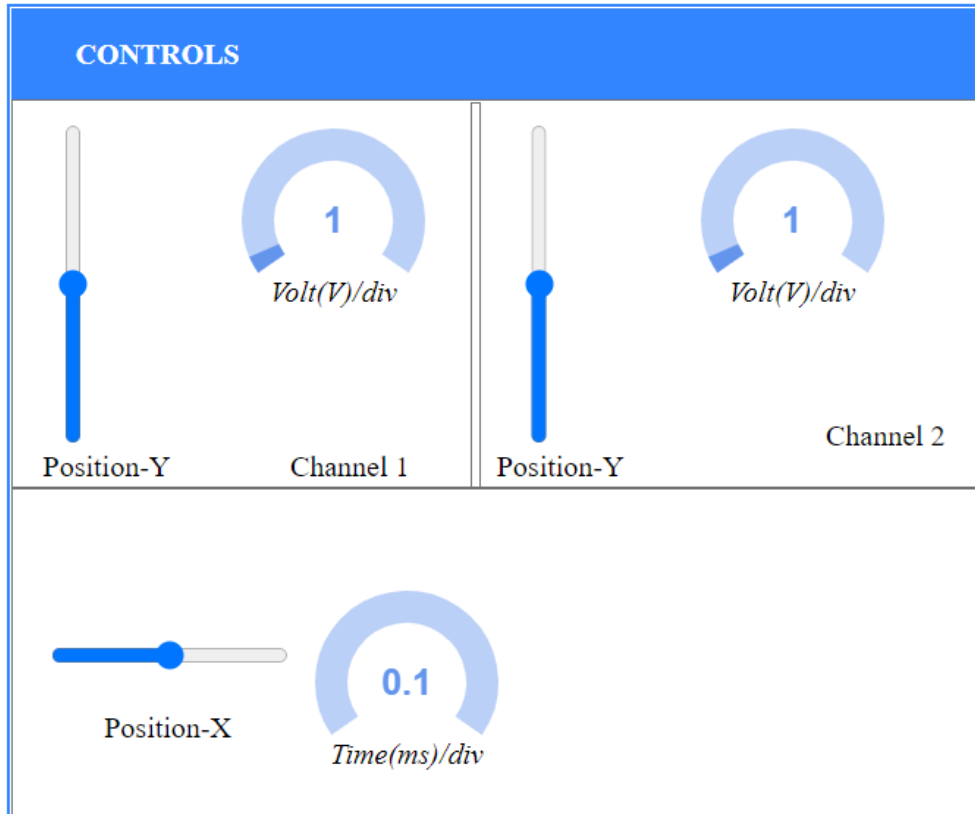


Figure 4: Controls

Oscilloscope

- * Channel 1(Input):
- * Channel 2(Output):

Figure 5: Oscilloscope Channel representation



Figure 6: Square Wave at Frequency = 1000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 1000) = 1\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 7: Square Wave at Frequency = 2000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 8: Square Wave at Frequency = 3000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 3000) = 0.333\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

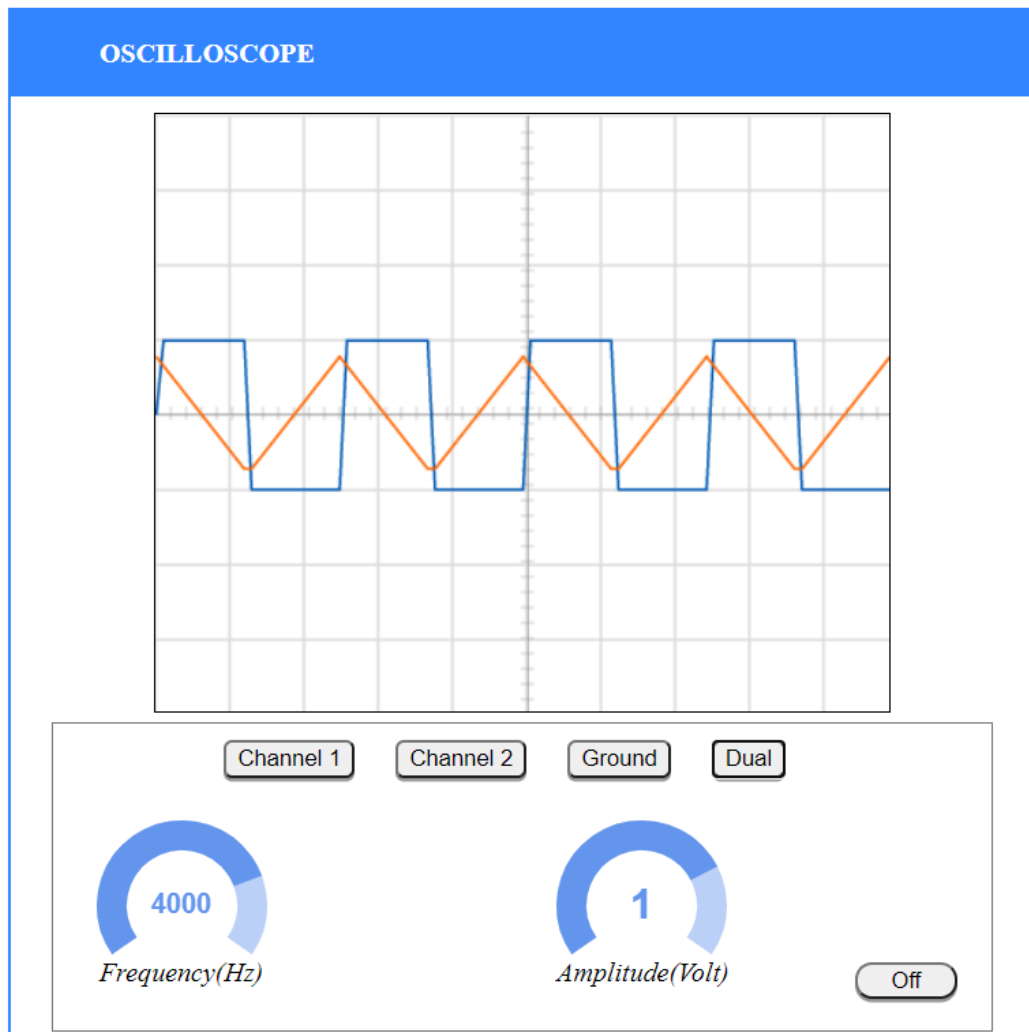


Figure 9: Square Wave at Frequency = 4000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 4000) = 0.25\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

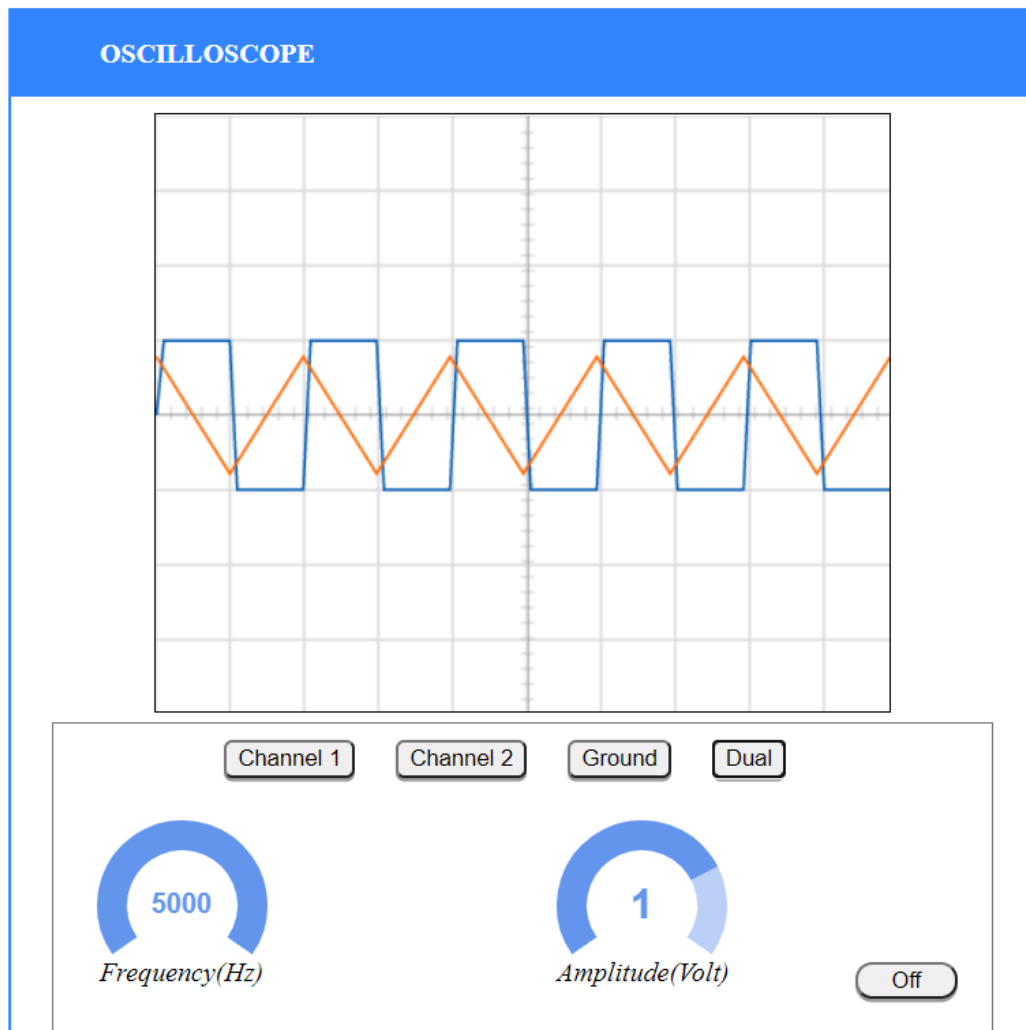


Figure 10: Square Wave at Frequency = 5000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 5000) = 0.2\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$