

**MP309**

Experiment 8

Half Wave Rectification

Name :- Patel Mihir Hemantkumar

Roll no. :- I18PH037

## List of Figures

1	Rectification . . . . .	3
2	Half Wave Rectification Circuit Diagram . . . . .	3
3	Half Wave Rectification . . . . .	4
4	Positive Half Cycle . . . . .	4
5	Negative Half Cycle . . . . .	4
6	Half Wave Rectifiers - Waveforms . . . . .	5
7	Half Wave Rectifier Circuit . . . . .	5
8	Circuit Connections . . . . .	6
9	Controls . . . . .	7
10	Oscilloscope Channel representation . . . . .	7
11	<i>Half Wave Rectifier for Frequency = 1000Hz</i> . . . . .	8
12	<i>Half Wave Rectifier for Frequency = 2000Hz</i> . . . . .	9
13	<i>Half Wave Rectifier for Frequency = 3000Hz</i> . . . . .	10
14	<i>Half Wave Rectifier for Frequency = 4000Hz</i> . . . . .	11
15	<i>Half Wave Rectifier for Frequency = 5000Hz</i> . . . . .	12
16	Calculation for $R_L = 100\Omega$ . . . . .	13
17	Calculation for $R_L = 200\Omega$ . . . . .	14
18	Calculation for $R_L = 300\Omega$ . . . . .	15
19	Calculation for $R_L = 400\Omega$ . . . . .	16
20	Calculation for $R_L = 500\Omega$ . . . . .	17
21	Calculation for $R_L = 600\Omega$ . . . . .	18
22	Calculation for $R_L = 700\Omega$ . . . . .	19
23	Calculation for $R_L = 800\Omega$ . . . . .	20
24	Calculation for $R_L = 900\Omega$ . . . . .	21
25	Calculation for $R_L = 1000\Omega$ . . . . .	22



Figure 1: A rectifier is a device that converts alternating current (AC) to direct current (DC), a process known as rectification. Rectifiers are essentially of two types – a half wave rectifier and a full wave rectifier.

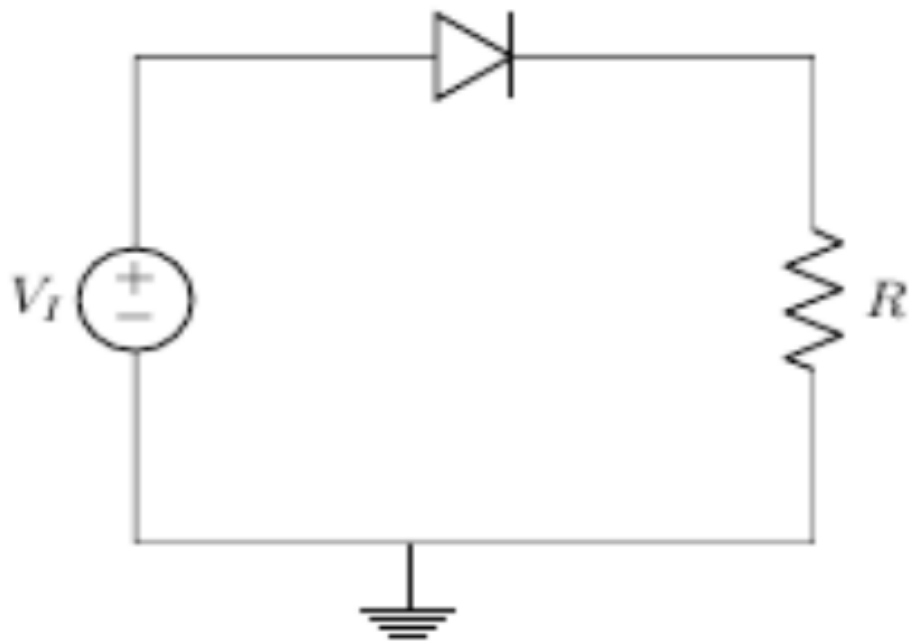


Figure 2: Half Wave Rectification Circuit Diagram

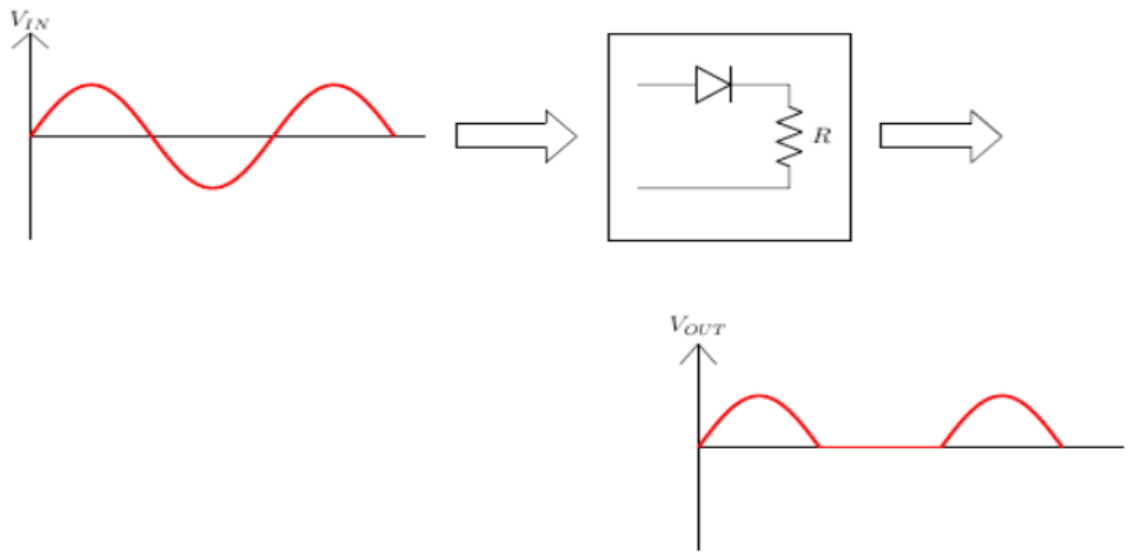


Figure 3: Half Wave Rectification

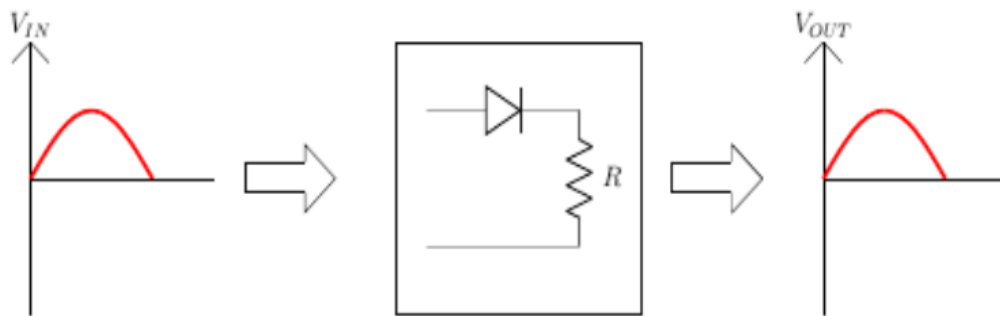


Figure 4: Positive Half Cycle

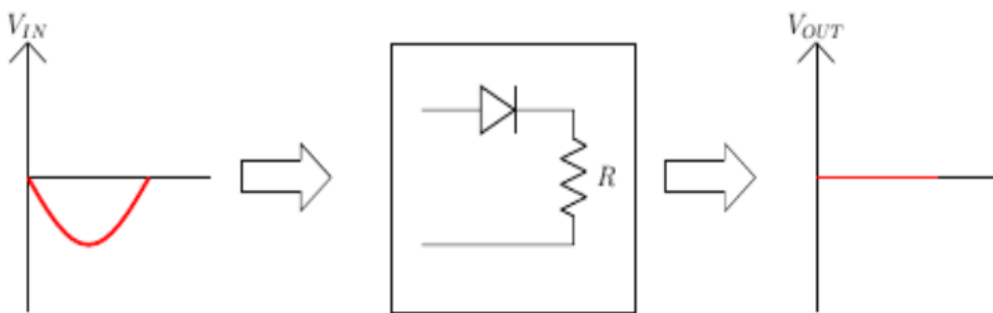


Figure 5: Negative Half Cycle

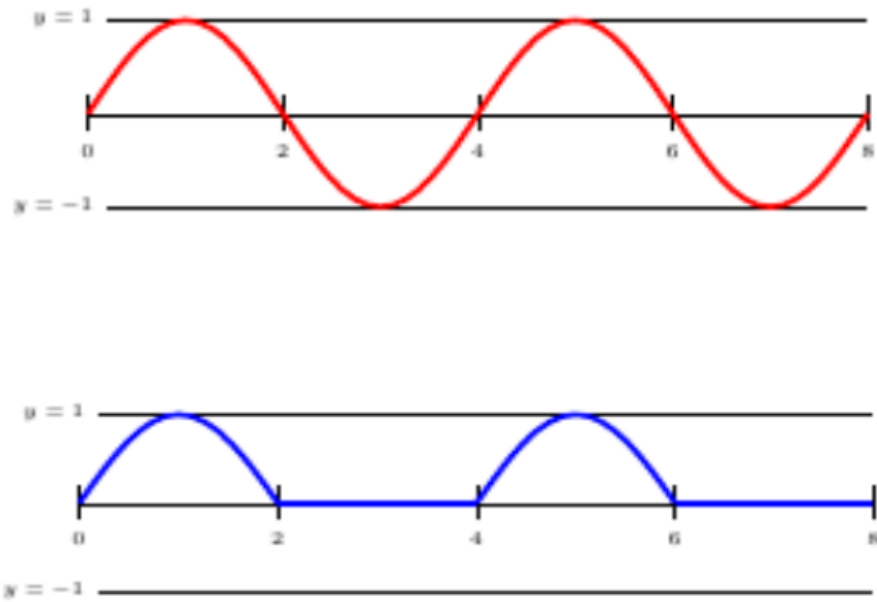


Figure 6: Half Wave Rectifiers - Waveforms

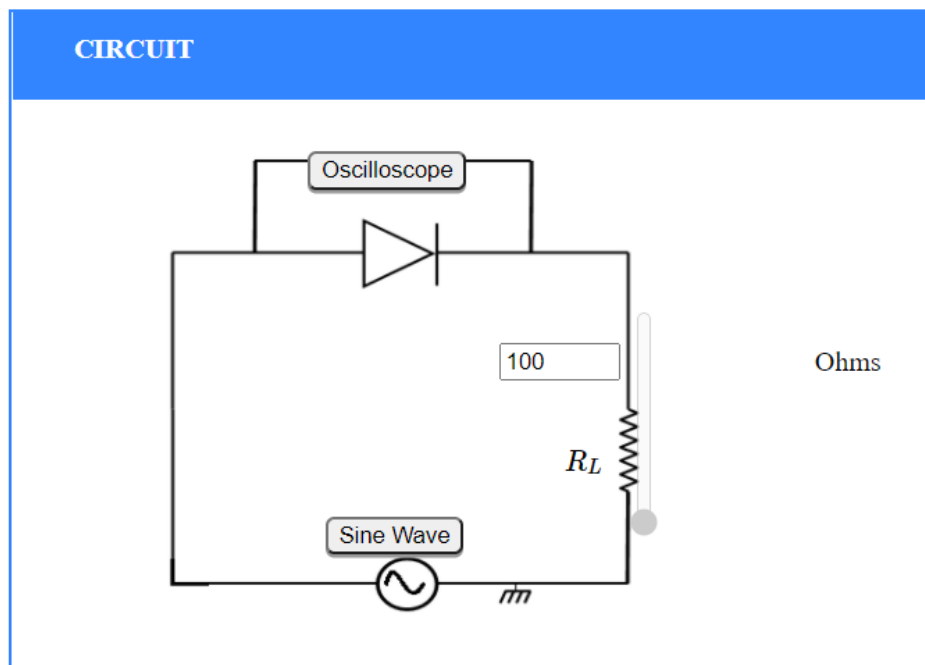


Figure 7: Half Wave Rectifier Circuit

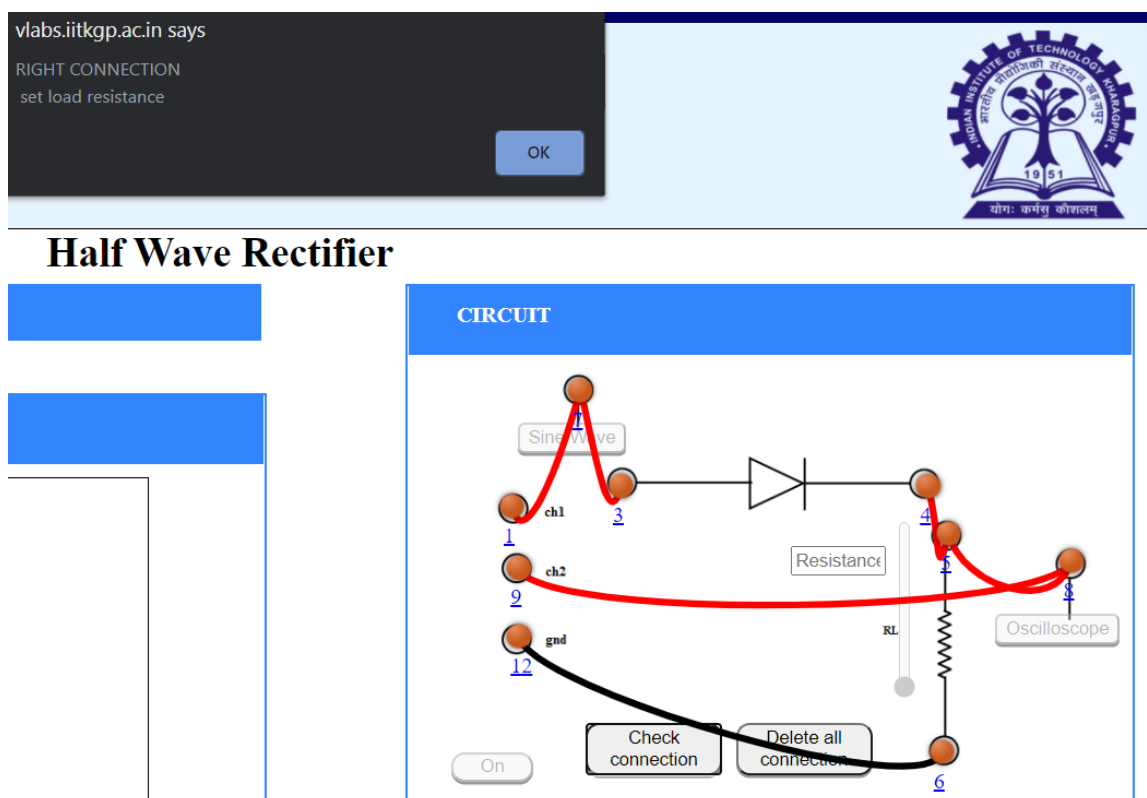


Figure 8: Circuit Connections

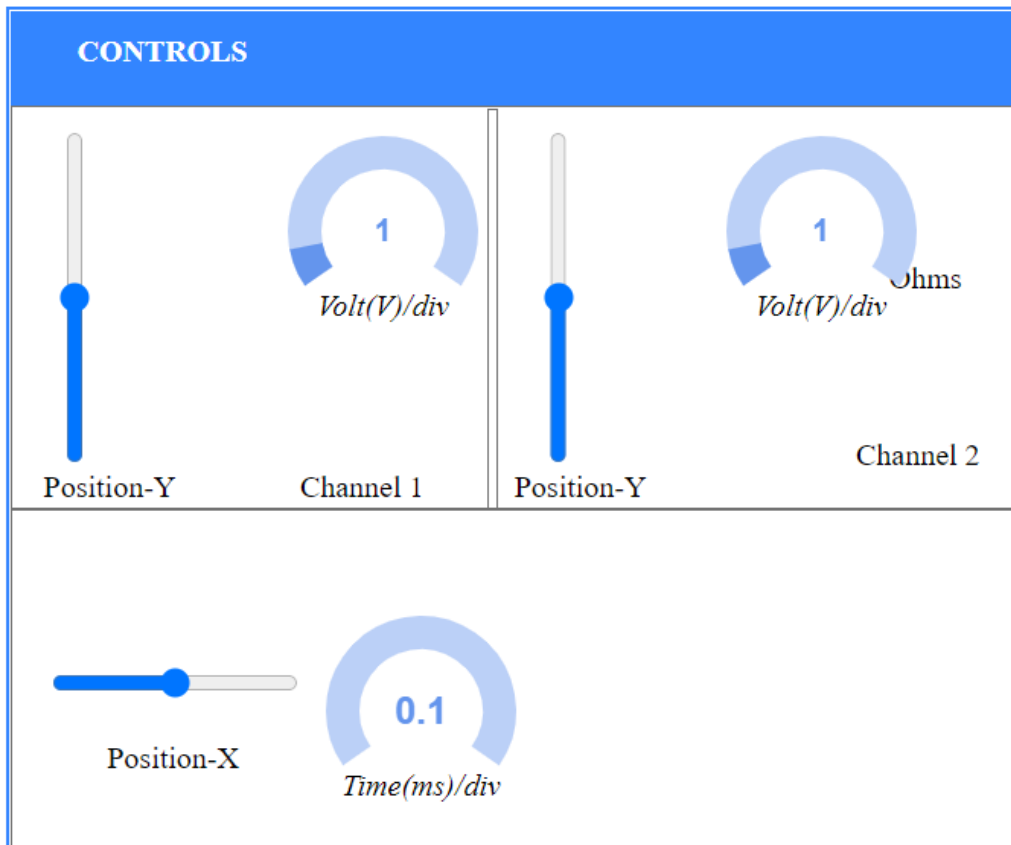


Figure 9: Controls

### Oscilloscope

- \* Channel 1(Input): \_\_\_\_\_
- \* Channel 2(Output): \_\_\_\_\_

Figure 10: Oscilloscope Channel representation



Figure 11: *Half Wave Rectifier for Frequency = 1000Hz*

$$Frequency = (1/TimePeriod)$$

$$Time\ Period = (1/frequency)$$

$$\text{i.e. } Time\ Period = (1/1000) = 1msec$$

$$Amplitude\ (Volt/div) = 1V$$

$$Time(ms)/div = 0.1ms$$





Figure 12: *Half Wave Rectifier for Frequency = 2000Hz*

$$\text{Time Period} = (1/\text{frequency})$$

$$\text{i.e. Time Period} = (1/2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1V$$

$$\text{Time(ms)/div} = 0.1\text{ms}$$



Figure 13: *Half Wave Rectifier for Frequency = 3000Hz*

$$Frequency = (1/TimePeriod)$$

$$Time\ Period = (1/frequency)$$

$$\text{i.e. } Time\ Period = (1/3000) = 0.333msec$$

$$Amplitude\ (Volt/div) = 1V$$

$$Time(ms)/div = 0.1ms$$

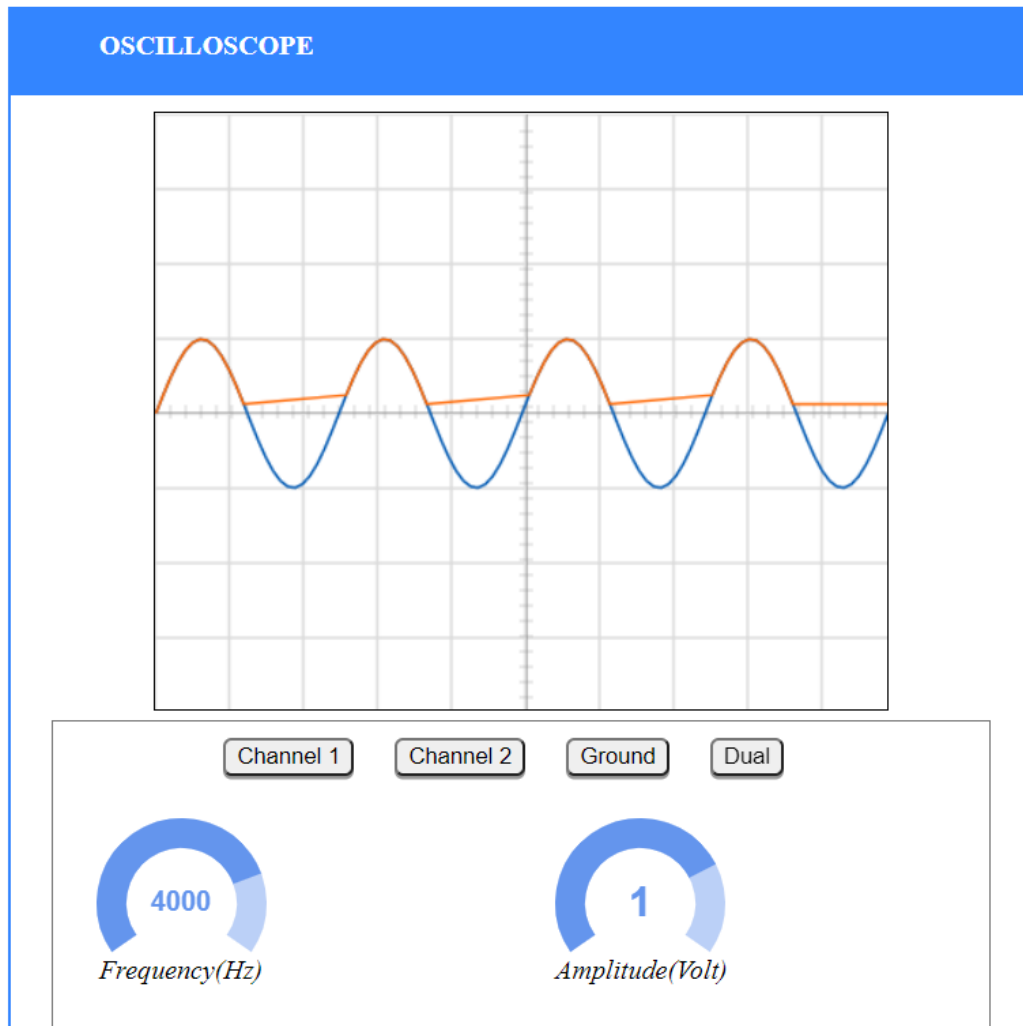


Figure 14: *Half Wave Rectifier for Frequency = 4000Hz*

$$Frequency = (1/TimePeriod)$$

$$Time\ Period = (1/frequency)$$

$$\text{i.e. } Time\ Period = (1/4000) = 0.25msec$$

$$Amplitude\ (Volt/div) = 1V$$

$$Time(ms)/div = 0.1ms$$



Figure 15: *Half Wave Rectifier for Frequency = 5000Hz*

$$Frequency = (1/TimePeriod)$$

$$Time\ Period = (1/frequency)$$

$$\text{i.e. } Time\ Period = (1/5000) = 0.2msec$$

$$Amplitude\ (Volt/div) = 1V$$

$$Time(ms)/div = 0.1ms$$

Figure 16: Calculation for  $R_L = 100\Omega$

CALCULATION	
$V_{rms} = \frac{V_m}{2}$ , $V_m$ is the peak voltage	
$V_{dc} = \frac{V_m}{\pi}$	
Ripple Factor = $\frac{V_{ac}}{V_{dc}}$ Since, $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$	
Peak Current:	<input type="text" value="2.9999999892691407"/> mA

1) *Peak Current*,  $I_m = 2.9999mA$

2) *Average DC Current*,  $I_{av} = I_m/\pi = 2.9999/3.1415 = 0.9549mA$

3) *RMS Current*,  $I_{rms} = I_m/2 = 2.9999/2 = 1.4999mA = 1.5mA$

4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (1.5A)^2 \times 100\Omega \times 10^{-6}$

i.e.  $P_{ac} = 225 \times 10^{-4}W$

5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.9549A)^2 \times 100\Omega \times 10^{-6}$

i.e.  $P_{dc} = 91.19 \times 10^{-4}W$

6) *Efficiency* =  $P_{dc}/P_{ac} \times 100 = 40.52\%$

7) *Ripple factor* =  $\sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((1.499 \times 10^{-3})/(0.954 \times 10^{-3}))^2 - 1}$

i.e. *Ripple factor* = 1.2090

Figure 17: Calculation for  $R_L = 200\Omega$

CALCULATION	
$V_{rms} = \frac{V_m}{2}$ , $V_m$ is the peak voltage	
$V_{dc} = \frac{V_m}{\pi}$	
Ripple Factor = $\frac{V_{ac}}{V_{dc}}$ Since, $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$	
Peak Current:	<input type="text" value="1.4999999946345703"/> mA

1) *Peak Current*,  $I_m = 1.499mA$

2) *Average DC Current*,  $I_{av} = I_m/\pi = 1.499/3.14 = 0.477mA$

3) *RMS Current*,  $I_{rms} = I_m/2 = 1.499/2 = 0.7495mA$

4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.7495A)^2 \times 200\Omega \times 10^{-6}$

i.e.  $P_{ac} = 1.123 \times 10^{-4}W$

5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.477A)^2 \times 200\Omega \times 10^{-6}$


i.e.  $P_{dc} = 0.455 \times 10^{-4}W$

6) *Efficiency* =  $P_{dc}/P_{ac} \times 100 = 40.5\%$

7) *Ripple factor* =  $\sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.7495 \times 10^{-3})/(0.477 \times 10^{-3}))^2 - 1}$

i.e. *Ripple factor* = 1.20

Figure 18: Calculation for  $R_L = 300\Omega$

**CALCULATION**


$V_{rms} = \frac{V_m}{2}$ ,  $V_m$  is the peak voltage

$V_{dc} = \frac{V_m}{\pi}$

Ripple Factor =  $\frac{V_{ac}}{V_{dc}}$     Since,  $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$

Peak Current:  mA

- 1) *Peak Current*,  $I_m = 0.999mA$
- 2) *Average DC Current*,  $I_{av} = I_m/\pi = 0.999/3.14 = 0.318mA$
- 3) *RMS Current*,  $I_{rms} = I_m/2 = 0.999/2 = 0.4995mA$
- 4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.4995A)^2 \times 300\Omega \times 10^{-6}$   
i.e.  $P_{ac} = 0.748 \times 10^{-4}W$
- 5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.318A)^2 \times 300\Omega \times 10^{-6}$   
i.e.  $P_{dc} = 0.303 \times 10^{-4}W$
- 6) *Efficiency* =  $P_{dc}/P_{ac} \times 100 = 40.5\%$
- 7) *Ripple factor* =  $\sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.4995 \times 10^{-3})/(0.318 \times 10^{-3}))^2 - 1}$   
i.e. *Ripple factor* = 1.20

Figure 19: Calculation for  $R_L = 400\Omega$

**CALCULATION**

$V_{rms} = \frac{V_m}{2}$ ,  $V_m$  is the peak voltage

$V_{dc} = \frac{V_m}{\pi}$

Ripple Factor  $= \frac{V_{ac}}{V_{dc}}$     Since,  $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$

Peak Current:  must

- 1) *Peak Current*,  $I_m = 0.7499mA$
- 2) *Average DC Current*,  $I_{av} = I_m/\pi = 0.7499/3.14 = 0.238mA$
- 3) *RMS Current*,  $I_{rms} = I_m/2 = 0.7499/2 = 0.375mA$
- 4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.375A)^2 \times 400\Omega \times 10^{-6}$   
i.e.  $P_{ac} = 0.562 \times 10^{-4}W$
- 5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.238A)^2 \times 400 \times 10^{-6}$   
i.e.  $P_{dc} = 0.226 \times 10^{-4}W$
- 6) *Efficiency*  $= P_{dc}/P_{ac} \times 100 = 40.21\%$
- 7) *Ripple factor*  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.375 \times 10^{-3})/(0.238 \times 10^{-3}))^2 - 1}$   
i.e. *Ripple factor*  $= 1.21$



Figure 20: Calculation for  $R_L = 500\Omega$

CALCULATION	
$V_{rms} = \frac{V_m}{2}$ , $V_m$ is the peak voltage	
$V_{dc} = \frac{V_m}{\pi}$	
Ripple Factor $= \frac{V_{ac}}{V_{dc}}$ Since, $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$	
Peak Current:	<input type="text" value="0.5999999978538282"/> must

1) *Peak Current*,  $I_m = 0.599mA$

2) *Average DC Current*,  $I_{av} = I_m/\pi = 0.599/3.14 = 0.190mA$

3) *RMS Current*,  $I_{rms} = I_m/2 = 0.599/2 = 0.2995mA$

4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.2995A)^2 \times 500\Omega \times 10^{-6}$

i.e.  $P_{ac} = 44.85 \times 10^{-3}W$

5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.19A)^2 \times 500\Omega \times 10^{-6}$

i.e.  $P_{dc} = 18.05 \times 10^{-6}W$

6) *Efficiency*  $= P_{dc}/P_{ac} \times 100 = 40.24\%$

7) *Ripple factor*  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.2995 \times 10^{-3})/(0.190 \times 10^{-3}))^2 - 1}$

i.e. *Ripple factor*  $= 1.21$

Figure 21: Calculation for  $R_L = 600\Omega$

CALCULATION	
$V_{rms} = \frac{V_m}{2}$ , $V_m$ is the peak voltage	
$V_{dc} = \frac{V_m}{\pi}$	
Ripple Factor $= \frac{V_{ac}}{V_{dc}}$ Since, $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$	
Peak Current:	<input type="text" value="0.4999999982115235"/> must

1) Peak Current,  $I_m = 0.499mA$

2) Average DC Current,  $I_{av} = I_m/\pi = 0.499/3.14 = 0.1589mA$

3) RMS Current,  $I_{rms} = I_m/2 = 0.499/2 = 0.249mA$

4) Input AC Power,  $P_{ac} = I_{rms}^2 \times R_L = (0.249A)^2 \times 600\Omega \times 10^{-6}$

i.e.  $P_{ac} = 37.2 \times 10^{-6}W$

5) Output DC Power,  $P_{dc} = I_{av}^2 \times R_L = (0.1589A)^2 \times 600\Omega \times 10^{-6}$


i.e.  $P_{dc} = 15.14 \times 10^{-6}W$

6) Efficiency  $= P_{dc}/P_{ac} \times 100 = 40.7\%$

7) Ripple factor  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.249 \times 10^{-3})/(0.1589 \times 10^{-3}))^2 - 1}$

i.e. Ripple factor  $= 1.20$

Figure 22: Calculation for  $R_L = 700\Omega$

CALCULATION	
$V_{rms} = \frac{V_m}{2}$ , $V_m$ is the peak voltage $V_{dc} = \frac{V_m}{\pi}$ Ripple Factor $= \frac{V_{ac}}{V_{dc}}$ Since, $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$	
Peak Current:	<input type="text" value="0.4285714270384487"/> must

1) Peak Current,  $I_m = 0.428mA$

2) Average DC Current,  $I_{av} = I_m/\pi = 0.428/3.14 = 0.136mA$

3) RMS Current,  $I_{rms} = I_m/2 = 0.428/2 = 0.214mA$

4) Input AC Power,  $P_{ac} = I_{rms}^2 \times R_L = (0.214A)^2 \times 700\Omega \times 10^{-6}$

i.e.  $P_{ac} = 32.05 \times 10^{-6}W$

5) Output DC Power,  $P_{dc} = I_{av}^2 \times R_L = (0.136A)^2 \times 700\Omega \times 10^{-6}$


i.e.  $P_{dc} = 12.94 \times 10^{-6}W$

6) Efficiency  $= P_{dc}/P_{ac} \times 100 = 40.3\%$

7) Ripple factor  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.214 \times 10^{-3})/(0.136 \times 10^{-3}))^2 - 1}$

i.e. Ripple factor  $= 1.21$

Figure 23: Calculation for  $R_L = 800\Omega$

**CALCULATION**


$V_{rms} = \frac{V_m}{2}$ ,  $V_m$  is the peak voltage


$V_{dc} = \frac{V_m}{\pi}$

Ripple Factor  $= \frac{V_{ac}}{V_{dc}}$     Since,  $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$

Peak Current:  must

- 1) *Peak Current*,  $I_m = 0.3749mA$
- 2) *Average DC Current*,  $I_{av} = I_m/\pi = 0.3749/3.14 = 0.119mA$
- 3) *RMS Current*,  $I_{rms} = I_m/2 = 0.3749/2 = 0.187mA$
- 4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.187A)^2 \times 800\Omega \times 10^{-6}$   
i.e.  $P_{ac} = 27.97 \times 10^{-6}W$
- 5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.119A)^2 \times 800\Omega \times 10^{-6}$   
i.e.  $P_{dc} = 11.32 \times 10^{-6}W$
- 6) *Efficiency*  $= P_{dc}/P_{ac} \times 100 = 40.4\%$
- 7) *Ripple factor*  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.187 \times 10^{-3})/(0.119 \times 10^{-3}))^2 - 1}$   
i.e. *Ripple factor*  $= 1.20$

Figure 24: Calculation for  $R_L = 900\Omega$

**CALCULATION**


$V_{rms} = \frac{V_m}{2}$ ,  $V_m$  is the peak voltage


$V_{dc} = \frac{V_m}{\pi}$

Ripple Factor  $= \frac{V_{ac}}{V_{dc}}$     Since,  $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$

Peak Current:  must

- 1) *Peak Current*,  $I_m = 0.333mA$
- 2) *Average DC Current*,  $I_{av} = I_m/\pi = 0.333/3.14 = 0.106mA$
- 3) *RMS Current*,  $I_{rms} = I_m/2 = 0.333/2 = 0.1665mA$
- 4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.1665A)^2 \times 900\Omega \times 10^{-6}$   
i.e.  $P_{ac} = 24.95 \times 10^{-6}W$
- 5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.106A)^2 \times 900\Omega \times 10^{-6}$   
i.e.  $P_{dc} = 10.11 \times 10^{-6}W$
- 6) *Efficiency*  $= P_{dc}/P_{ac} \times 100 = 40.5\%$
- 7) *Ripple factor*  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.1665 \times 10^{-3})/(0.106 \times 10^{-3}))^2 - 1}$   
i.e. *Ripple factor*  $= 1.2$

Figure 25: Calculation for  $R_L = 1000\Omega$

CALCULATION	
$V_{rms} = \frac{V_m}{2}$ , $V_m$ is the peak voltage  $V_{dc} = \frac{V_m}{\pi}$ Ripple Factor $= \frac{V_{ac}}{V_{dc}}$ Since, $V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$	
Peak Current: <span style="border: 1px solid black; padding: 2px 10px;">0.2999999989269141</span> must	

1) *Peak Current*,  $I_m = 0.299mA$

2) *Average DC Current*,  $I_{av} = I_m/\pi = 0.299/3.14 = 0.095mA$

3) *RMS Current*,  $I_{rms} = I_m/2 = 0.299/2 = 0.149mA$

4) *Input AC Power*,  $P_{ac} = I_{rms}^2 \times R_L = (0.149A)^2 \times 1000\Omega \times 10^{-6}$

i.e.  $P_{ac} = 22.5 \times 10^{-6}W$

5) *Output DC Power*,  $P_{dc} = I_{av}^2 \times R_L = (0.095)^2 \times 1000\Omega \times 10^{-6}$

i.e.  $P_{dc} = 9.025 \times 10^{-6}W$

6) *Efficiency*  $= P_{dc}/P_{ac} \times 100 = 40.3\%$

7) *Ripple factor*  $= \sqrt{(I_{rms}/I_{av})^2 - 1} = \sqrt{((0.149 \times 10^{-3})/(0.095 \times 10^{-3}))^2 - 1}$

i.e. *Ripple factor*  $= 1.2$