

MP309

Experiment 6

**Study of Differentiator and Integrator
using Operational Amplifier**

Name :- Patel Mihir Hemantkumar

Roll no. :- I18PH037

Part 1 :- Integrator using Opamp



Figure 1: Oscilloscope



Figure 2: Oscilloscope Probe

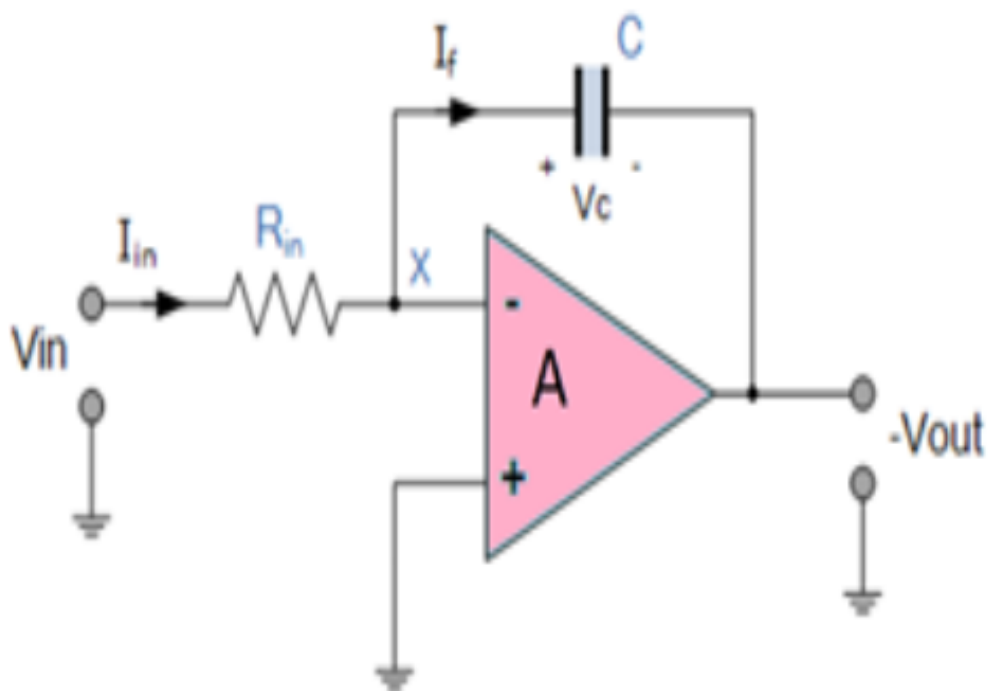


Figure 3: Integrator Circuit

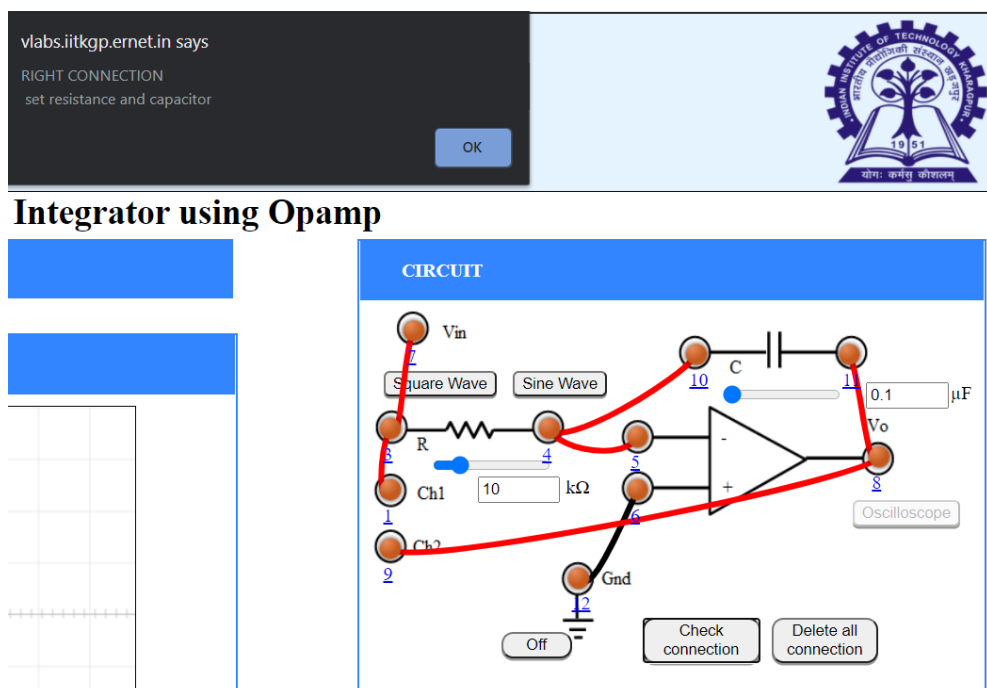


Figure 4: Integrator Circuit Connections

Initial Parameters :-

- Resistance(R) = $10\text{ k}\Omega$
- Capacitance(C) = $0.1\text{ }\mu\text{F}$

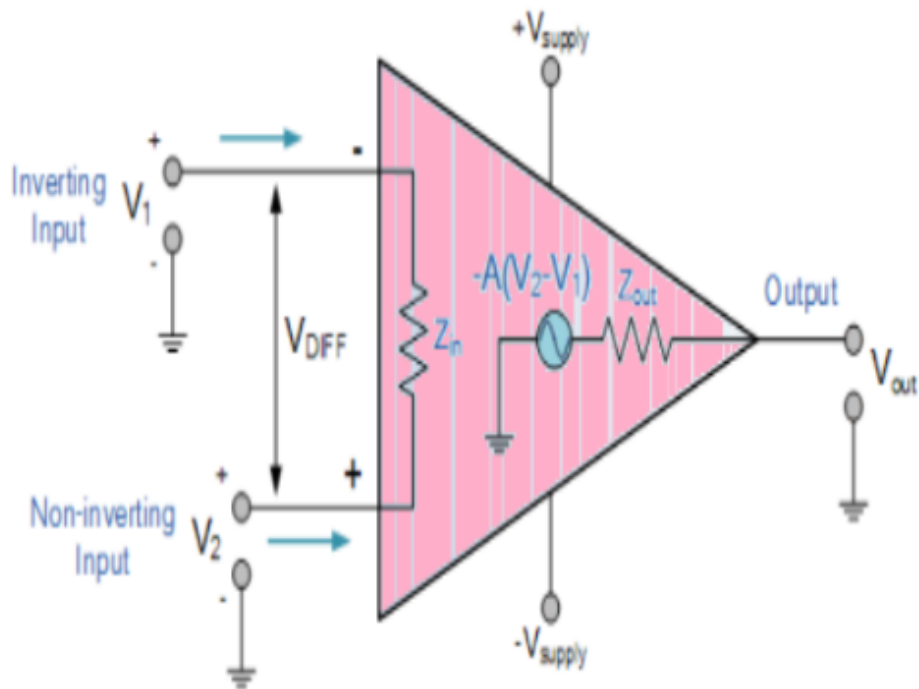


Figure 5: Operational Amplifier

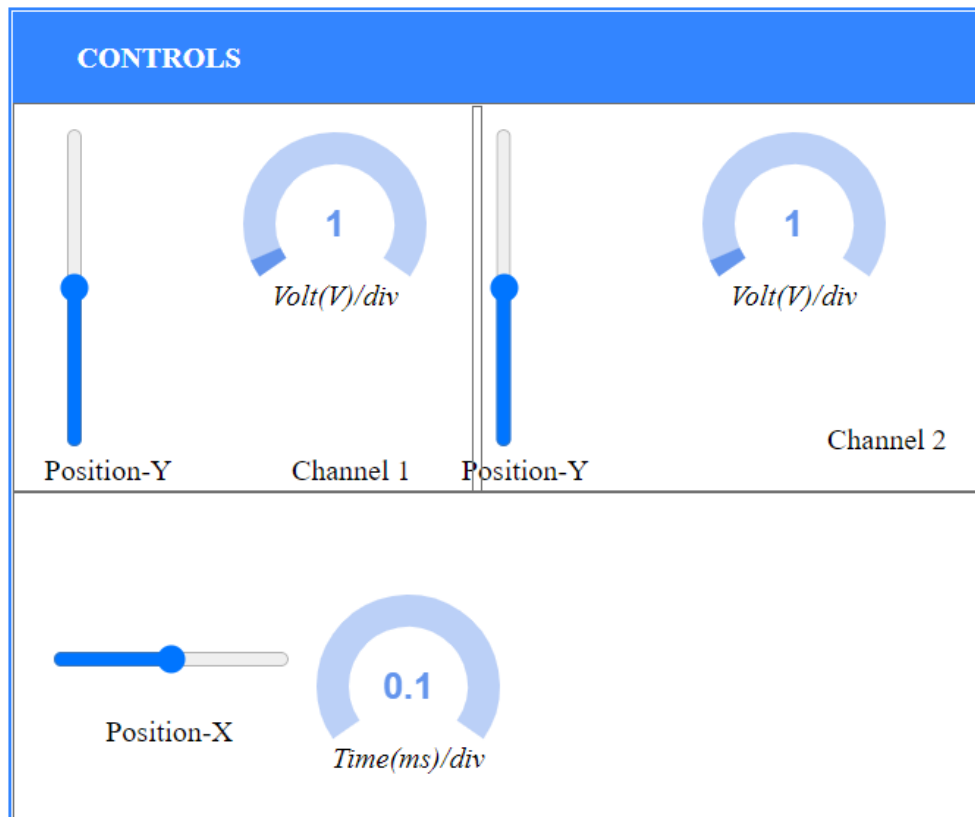


Figure 6: Controls

Oscilloscope

- * Channel 1(Input):
- * Channel 2(Output):

Figure 7: Oscilloscope Channel representation



Figure 8: Square Wave at Frequency = 1000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 1000) = 1\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 9: Square Wave at Frequency = 2000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 10: Square Wave at Frequency = 3000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 3000) = 0.333\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 11: Square Wave at Frequency = 4000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 4000) = 0.25\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 12: Square Wave at Frequency = 5000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 5000) = 0.2\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 13: Sine Wave at Frequency = 1000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 1000) = 1\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 14: Sine Wave at Frequency = 2000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

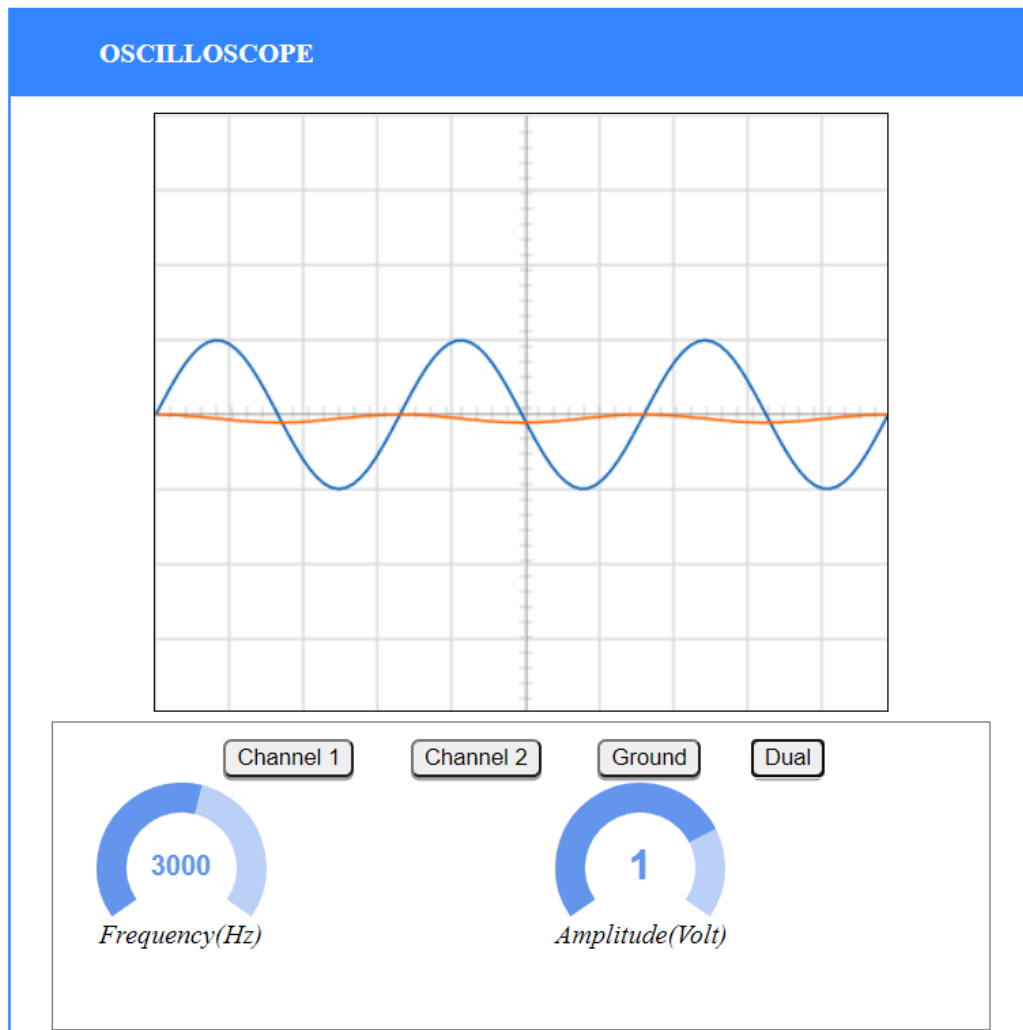


Figure 15: Sine Wave at Frequency = 3000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 3000) = 0.333\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

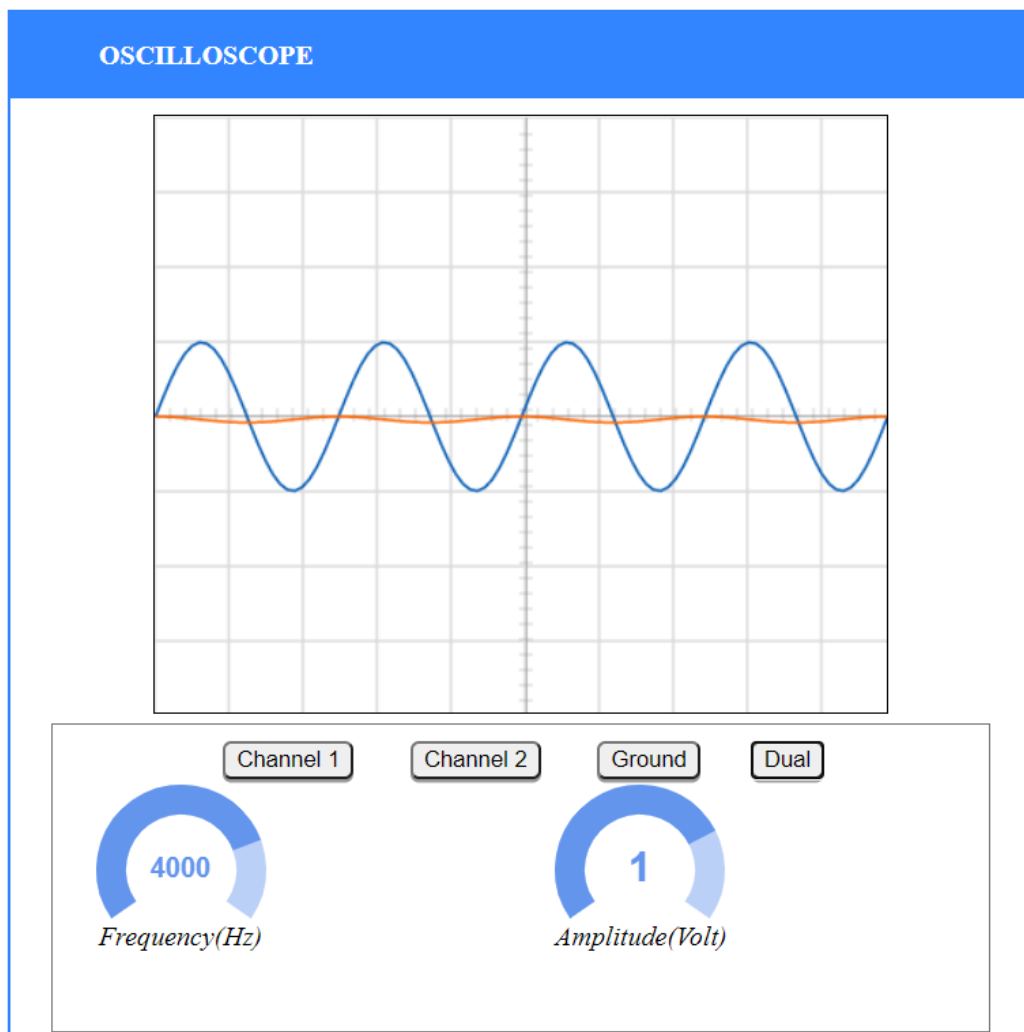


Figure 16: Sine Wave at Frequency = 4000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 4000) = 0.25\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

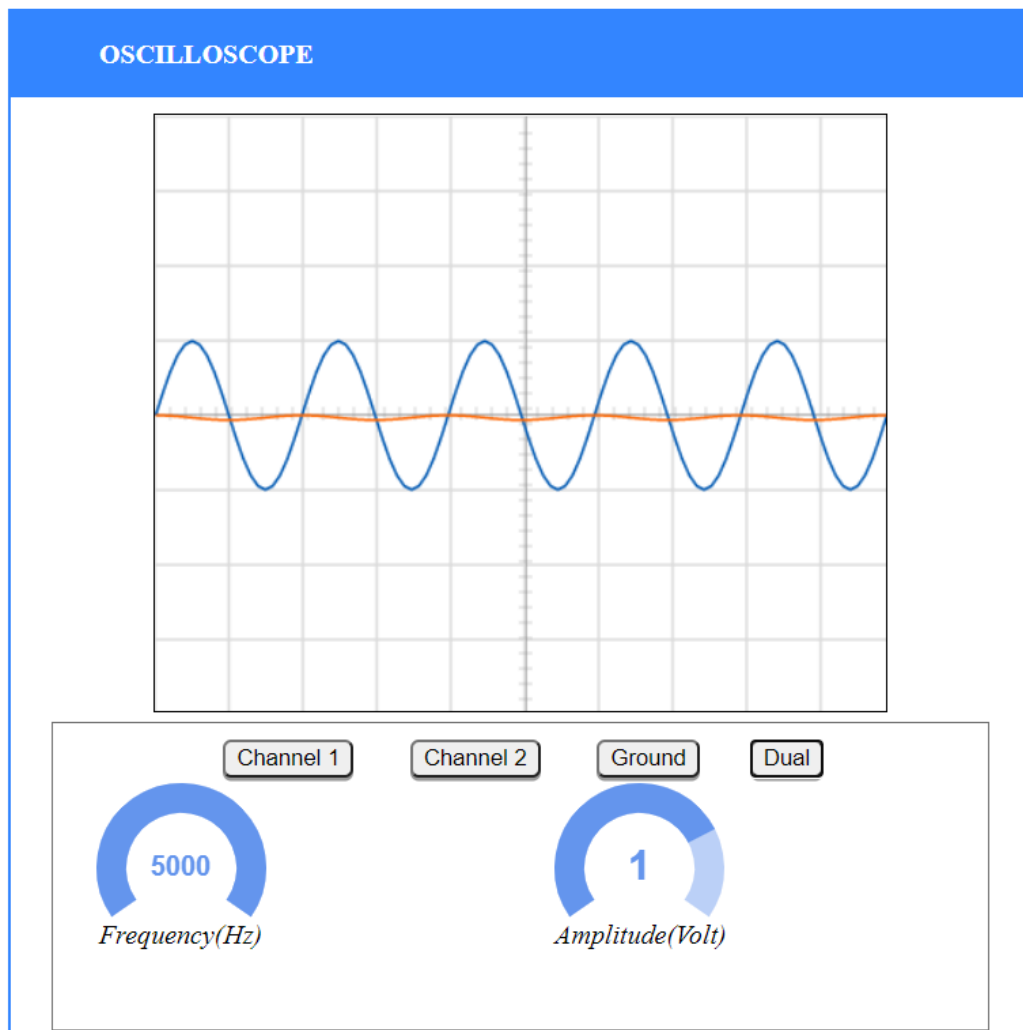


Figure 17: Sine Wave at Frequency = 5000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 5000) = 0.2\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

Part 2 :- Differentiator using Opamp


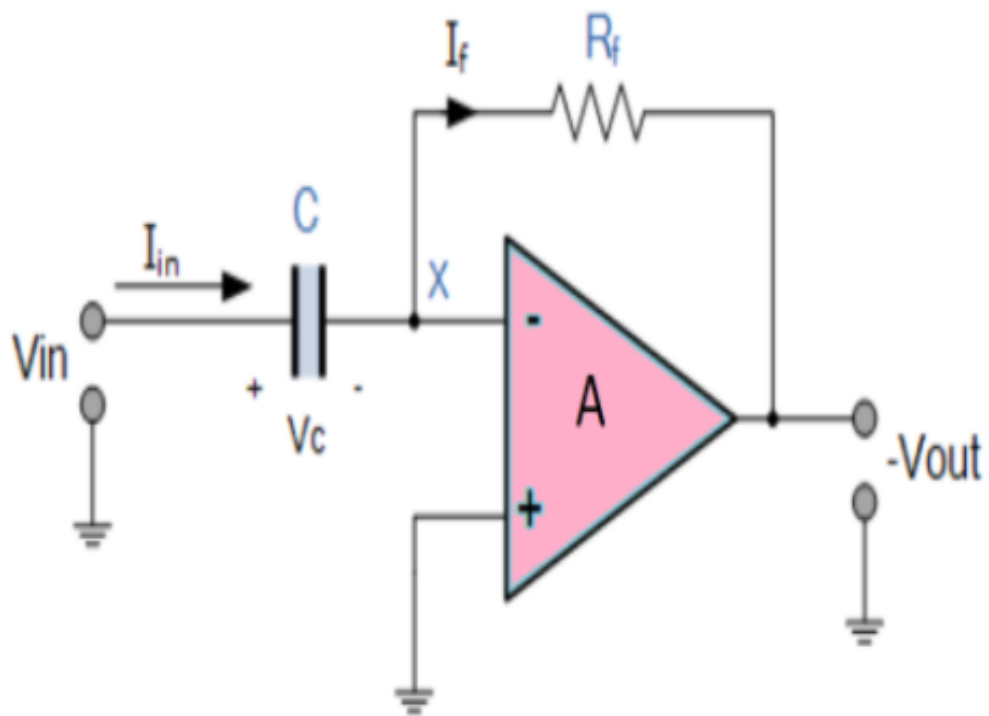


Figure 1: Differentiator Circuit

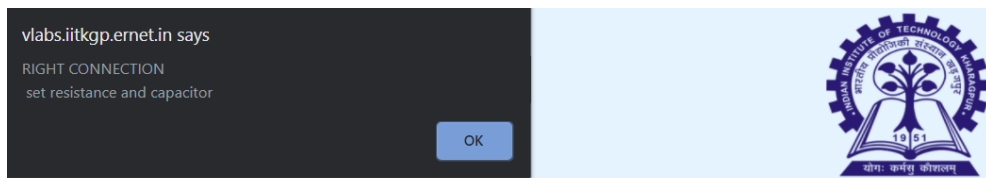

Differentiator using Opamp

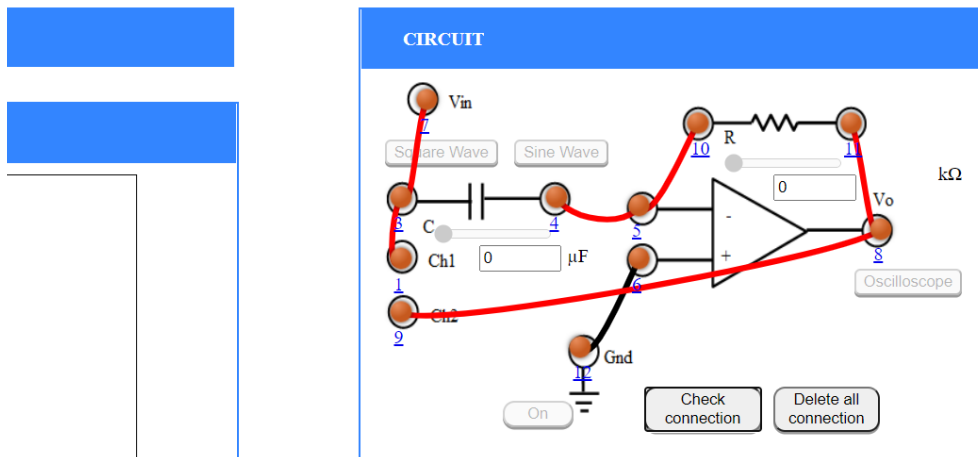


Figure 2: Differentiator Circuit Connections

Initial Parameters :-

- Resistance(R) = $1\text{ k}\Omega$
- Capacitance(C) = $0.1\text{ }\mu\text{F}$

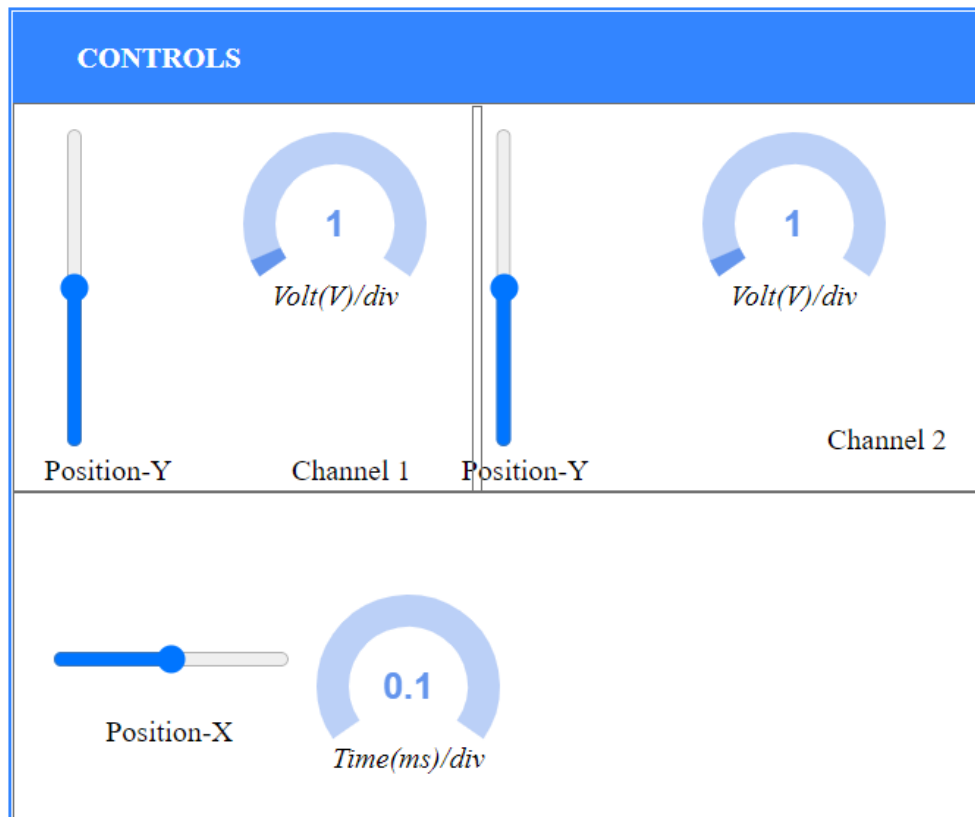


Figure 3: Controls

Oscilloscope

- * Channel 1(Input):
- * Channel 2(Output):

Figure 4: Oscilloscope Channel representation



Figure 5: Square Wave at Frequency = 1000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 1000) = 1\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

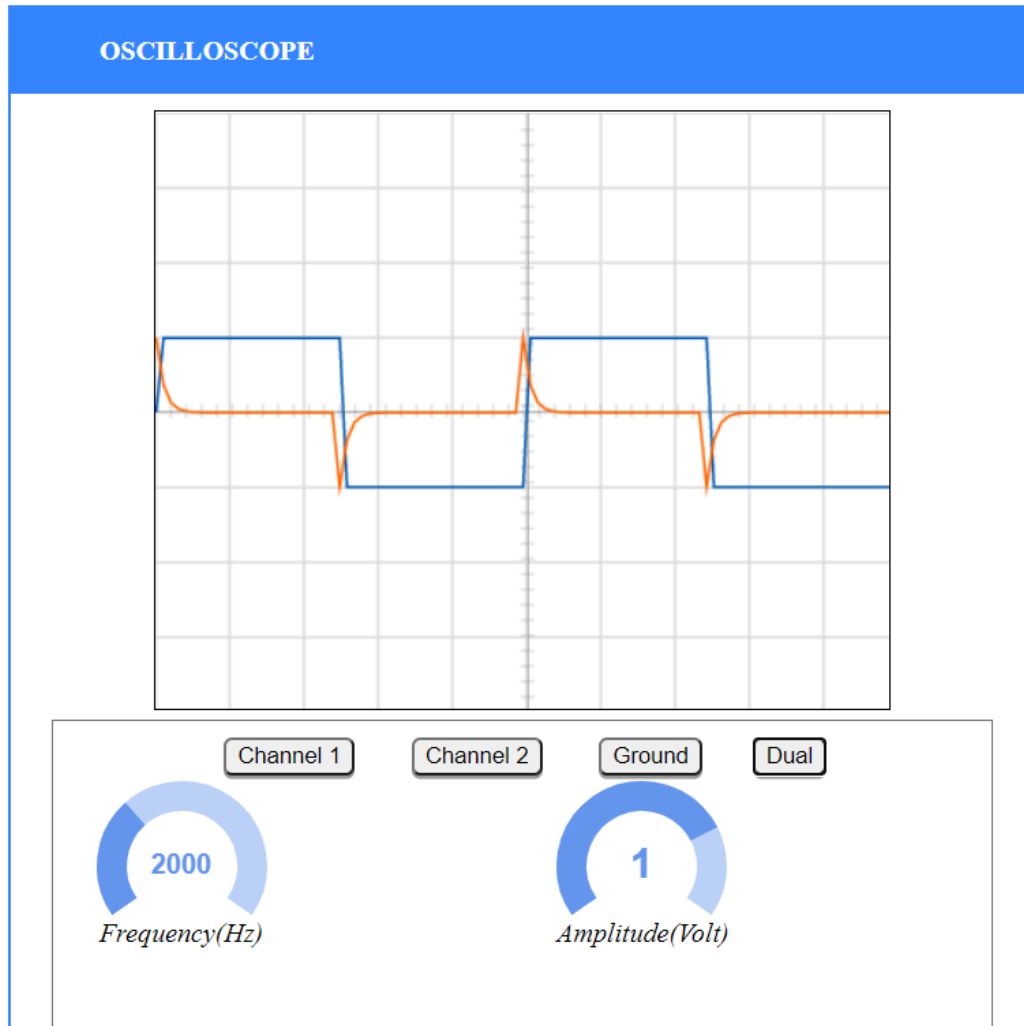


Figure 6: Square Wave at Frequency = 2000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 7: Square Wave at Frequency = 3000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 3000) = 0.333\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 8: Square Wave at Frequency = 4000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 4000) = 0.25\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 9: Square Wave at Frequency = 5000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 5000) = 0.2\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

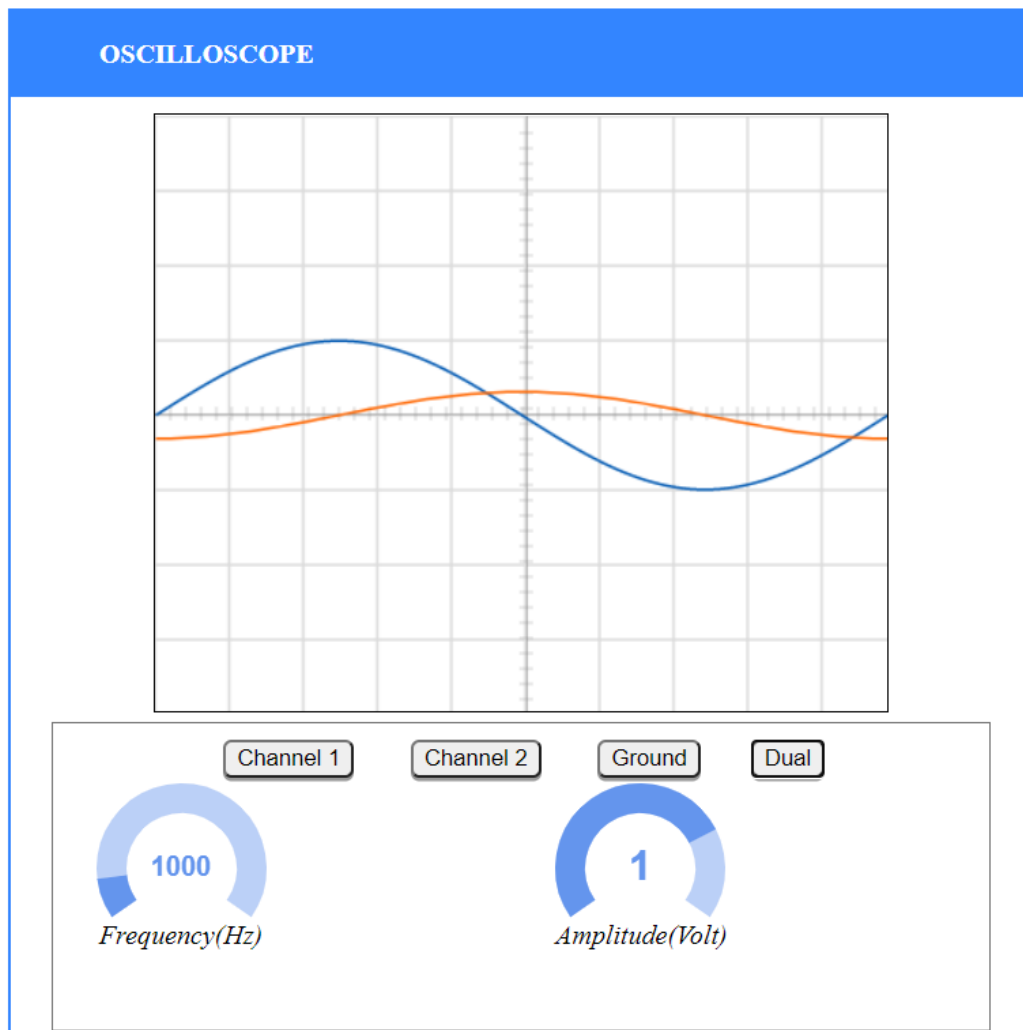


Figure 10: Sine Wave at Frequency = 1000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 1000) = 1\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$



Figure 11: Sine Wave at Frequency = 2000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 2000) = 0.5\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

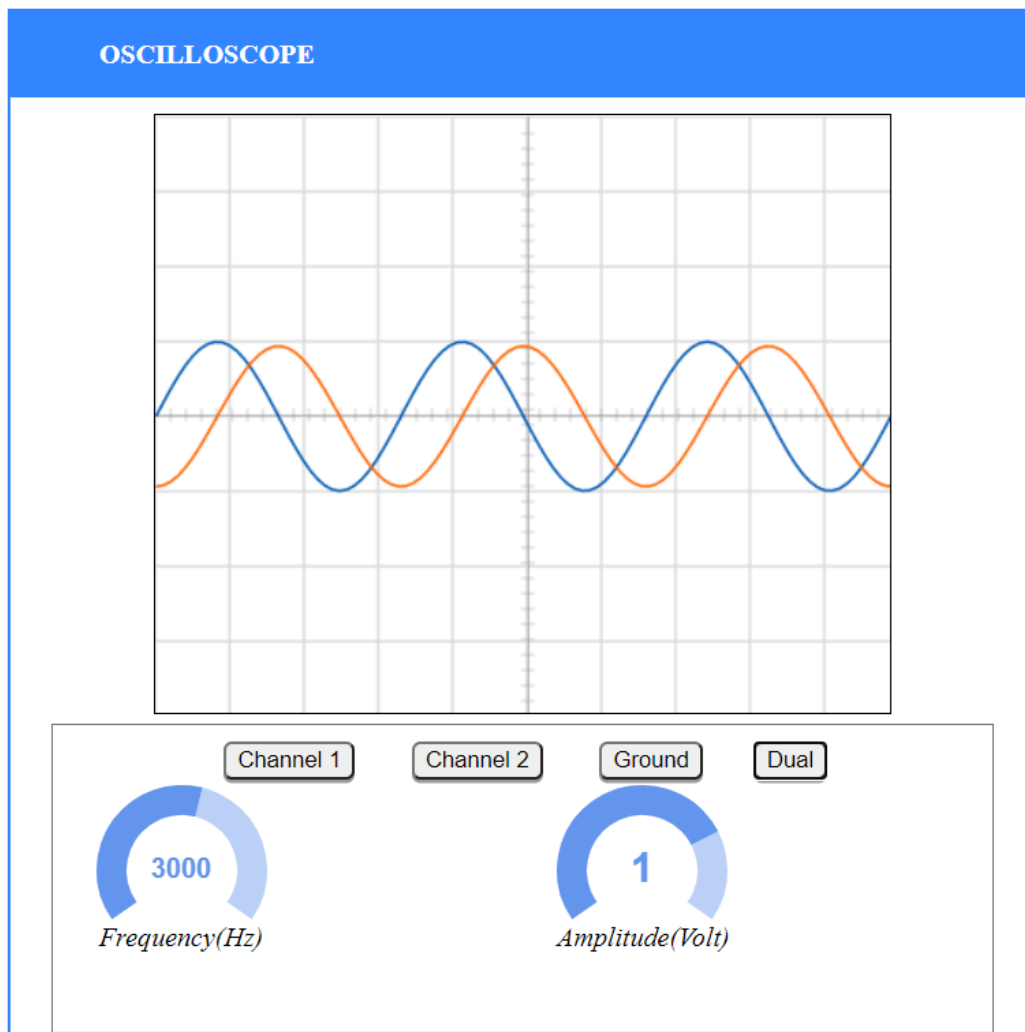


Figure 12: Sine Wave at Frequency = 3000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 3000) = 0.333\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

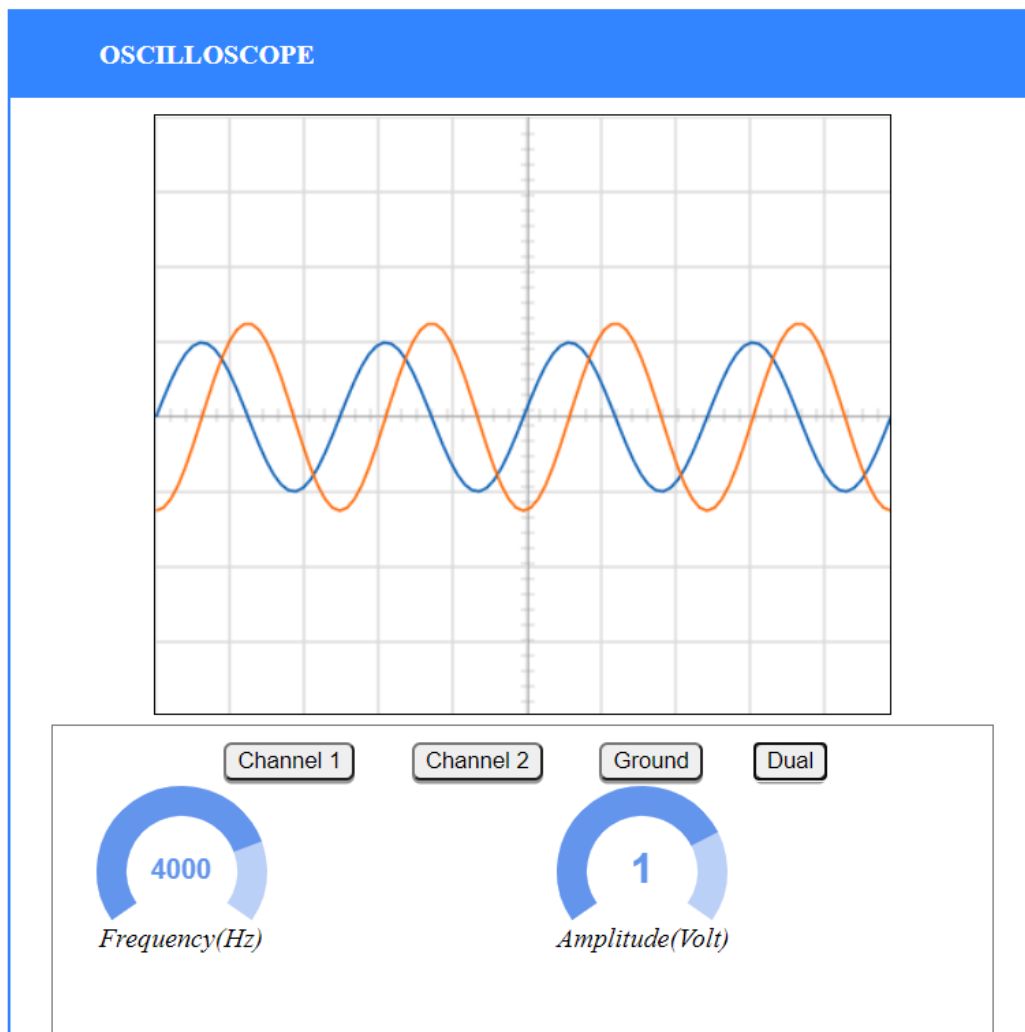


Figure 13: Sine Wave at Frequency = 4000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 4000) = 0.25\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$

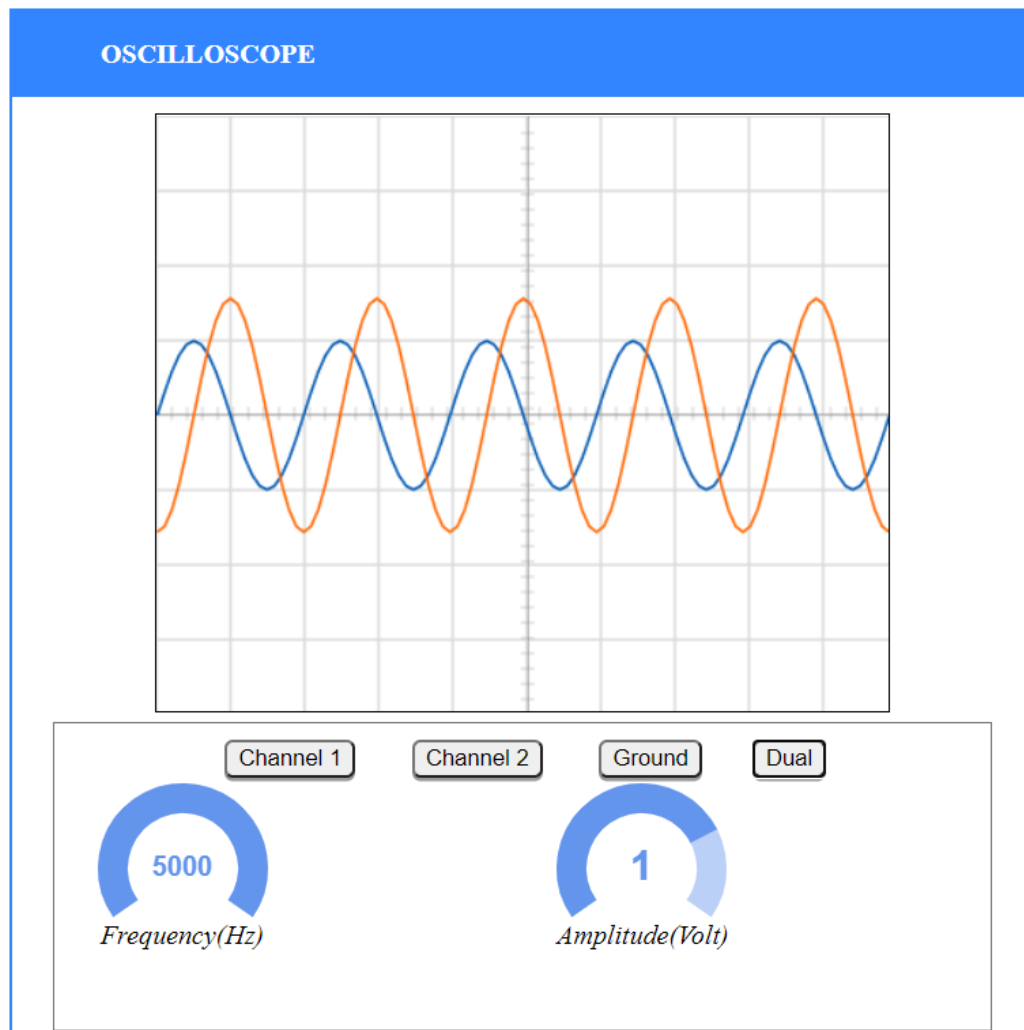


Figure 14: Sine Wave at Frequency = 5000

$$\text{Frequency} = (1 / \text{Time Period})$$

$$\text{Time Period} = (1 / \text{frequency})$$

$$\text{Time Period} = (1 / 5000) = 0.2\text{msec}$$

$$\text{Amplitude (Volt/div)} = 1 \text{ V}$$

$$\text{Time(ms)/div} = 0.1 \text{ ms}$$